AQA GCSE Physics | 8463

SPECIFICATION POINT 4.2.1.1

Standard circuit diagram symbols

Mark schemes and examiner comments

Tier	**Foundation**
Question groups	**24**
Available paper years	**2003–2025**

Using this booklet

1. Booklet answer numbers match the question booklet.
2. Use the original question number within marking tables.
3. Examiner comments are included where available.


Name: _____ **Date:** _____

Where a precise marking extract is unavailable, the full source document is included in an appendix. Any missing mark scheme is explicitly identified.

4.2.1.1 Standard circuit diagram symbols




Answer 01 · Mark scheme

June 2003 | 3451F | Original Q1 | Legacy

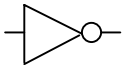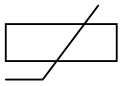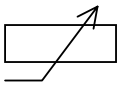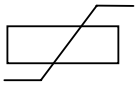(b)(i)	1 0 **or** 0 1 0 1 1 0 do **not** credit on / off responses		1
(ii)		accept mirror image accept  accept with either or both parts shaded accept line through as shading	1
(c)		accept off for 0 and on for 1 throughout	
	0 0	both correct	1
	0 1	both correct	1
	1 1	both correct	1
	1 1	both correct	1

4.2.1.1 Standard circuit diagram symbols

3451/F Q9 continued

(d)(i)		accept mirror image **or** inverted do **not** credit  **or**  or similar	1
(ii)	resistance decreases / increases / changes current (through it) increases / decreases / changes **or** temperature changes / increases / decreases (1) resistance changes / decreases / increases (1) (NTC thermistor) both marks independent but must be compatible to score **2** marks	accept 'voltage across it decreases' for **2** marks but only if it is made clear that this refers to a thermistor in series	1 1
total			13

4.2.1.1 Standard circuit diagram symbols

Answer 01 · Mark scheme June 2003 | 3451F | Original Q1 | Legacy

3451/F Q10

question	answers	extra information	mark
(a)(i)	friction	accept any way of indicating the correct answer	1
(ii)	gravity	accept any way of indicating the correct answer	1
(b)(i)	accelerates **or** speed / velocity increases	accept faster and faster (**1** mark) do **not** accept faster pace / falls faster or suggestions of a greater but constant speed	1
	downwards / falls	accept towards the Earth / ground this may score in part (b)(ii) if it does not score here and there is no contradiction between the two parts	1
(ii)	constant speed / velocity **or** terminal velocity / speed **or** zero acceleration	stays in the same place negates credit	1
total			5

4.2.1.1 Standard circuit diagram symbols

Answer 01 · Mark scheme June 2003 | 3451F | Original Q1 | Legacy

3451/F Q11

question	answers	extra information	mark
(a)(i)	X – mantle		1
	Y – inner core	do **not** accept solid core	1
(ii)	different to the crust **or** contains a lot of (heavy) metals	accept iron and nickel for metals	1
	higher (average) density **or** denser	density higher than 5500 (kg/m^3) gets **2** marks	1
(b)	animals were able to move from one continent to the other		1
	(when bridge broke) animals evolved differently	accept animals adapted differently	1
(c)(i)	earthquakes occur at the boundary between plates **or** earthquakes occur where plates push against each other		1
	there are no plate boundaries running through Britain	accept Britain is not near the edge of a plate	1
(ii)	convection currents (in the mantle) **or** heat released by (natural) radioactive processes		1
total			9

4.2.1.1 Standard circuit diagram symbols

3451/F Q12

question	answers	extra information	mark
(a)(i)	outside the Earth **or** not from the Earth	accept alien accept life from / on another planet / space accept our planet for Earth	1
(ii)	radio telescope(s)	do **not** accept telescopes do **not** accept satellite dishes do **not** accept radio receivers **or** transmitters	1
(b)(i)	galaxies	do **not** accept stars	1
(ii)	any **one** from: the pulses were regular pulses from space are usually random (scientists) thought technology had been used to produce the pulses neutron stars were unknown signals from a single point	 accept signals / beats for pulses accept noise for random pulses idea of regular but not continuous	1
(iii)	neutron star is (the matter / mass) left behind after a star / red giant explodes (as a super nova)	 accept after a super nova (explosion) neutron star causing super nova gets no credit	1 1
(c)(i)	carried on the balloon / equipment	accept carried by a rocket / aircraft / satellite birds negates credit	1
(ii)	on comets or meteors	accept meteorites / shooting stars accept returning space craft accept solar wind ignore asteroids accept ufo do **not** accept solar flares do **not** accept satellites	1
total			8

4.2.1.1 Standard circuit diagram symbols

Answer 01 · Mark scheme June 2003 | 3451F | Original Q1 | Legacy

3451/F Q13

question	answers	extra information	mark
(a)	silver is a (good) reflector of heat (radiation) **or** silver reflects the heat (radiation)	fact heat = infra red ignore references to light accept shiny for silver good radiator negates the mark ignore references to good conductor do **not** accept bounce back	1
	less heat is lost through the board **or** more heat is retained by the shirt	explanation accept both sides of shirt heated reflects heat back up gets **1** mark only ignore mention of friction	1
(b)	metal soleplate	accept soleplate / bottom / metal do **not** accept outside / case	1
(c)	plastic **or** rubber	accept any named plastic do **not** accept wood	1
	it is a (good) insulator **or** it is a poor conductor	ignore mention of heat if in conjunction with electricity	1
(d)	**Quality of written communication** *The answer to this question requires ideas in good English in a sensible order with correct use of scientific terms. Quality of written communication should be considered in crediting points in the mark scheme.*	*Maximum of **2** marks if ideas not well expressed.*	
	pulls iron bolt down **or** attracts the iron bolt **or** moves bolt out of plunger	answers in terms of charges attracting or repelling gain no credit	1
	plunger pushed / moved to the right (by spring) **or** plunger released		1
	push switch opens / goes to off / goes to right	accept circuit is broken for maximum credit the points must follow a logical sequence 3 correct points but incorrect sequence scores **2** marks only ignore reset action	1
total			8

4.2.1.1 Standard circuit diagram symbols

Answer 01 · Mark scheme June 2003 | 3451F | Original Q1 | Legacy

3451/F Q14

question	answers	extra information	mark
(a)(i)	any **one** from:		1
	the ground	do **not** accept mobile phones	
	the air		
	radon (gas)		
	building materials		
	buildings		
	rocks / granite		
	food		
	cosmic rays **or** solar rays	accept from outer space accept sun but **not** sunlight	
	X-rays	accept medical uses	
	nuclear weapons testing		
	nuclear power stations / accidents		

Answer 02 · Mark scheme June 2003 | 3462F3 | Original Q1 | Legacy

The full source mark scheme begins on page 42. Follow original question 1 in that document.

Answer 03 · Mark scheme June 2004 | 3451F | Original Q7 | Legacy

The full source mark scheme begins on page 59. Follow original question 7 in that document.

Answer 04 · Mark scheme June 2004 | 3451F | Original Q10 | Legacy

The full source mark scheme begins on page 59. Follow original question 10 in that document.

4.2.1.1 Standard circuit diagram symbols

Answer 05 · Mark scheme

June 2004 | 3451F | Original Q15 | Legacy

The full source mark scheme begins on page 59. Follow original question 15 in that document.

Answer 06 · Mark scheme

June 2004 | 3462F3 | Original Q8 | Legacy

The full source mark scheme begins on page 80. Follow original question 8 in that document.

Answer 07 · Mark scheme

June 2005 | 3451 | Original Q9 | Legacy

The full source mark scheme begins on page 97. Follow original question 9 in that document.

Answer 08 · Mark scheme



June 2006 | 3451 | Original Q10 | Legacy

The full source mark scheme begins on page 115. Follow original question 10 in that document.

4.2.1.1 Standard circuit diagram symbols

Answer 09 · Mark scheme January 2008 | PHY2F | Original Q6 | Legacy

Question 6

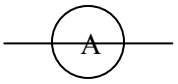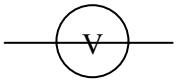question	answers	extra information	mark
(a)(i)	ammeter symbol correct and drawn in series	accept  do **not** accept lower case a	1
	voltmeter symbol correct and drawn in parallel with the material	do **not** accept 	1
(ii)	adjust / use the variable resistor **or** change the number of cells	accept change the resistance accept battery for cell accept change the p.d / accept change the voltage accept increase / decrease for change	1
(b)(i)	data is continuous (variable)		1
(ii)	36 (Ω)	correct answer only	1
(iii)	5.4 or their (b)(ii) × 0.15	allow **1** mark for correct substitution	2
(c)(i)	the thicker the putty the lower the resistance	answer must be comparative accept the converse	1

4.2.1.1 Standard circuit diagram symbols

PHY2F

Question 6 continued

question	answers	extra information	mark
(ii)	any **one** from: • measuring length incorrectly • measuring current incorrectly • measuring voltage incorrectly • ammeter / voltmeter incorrectly calibrated • thickness of putty not uniform • meter has a zero error	 accept may be different length do **not** accept different currents do **not** accept different voltage accept any sensible source of error eg putty at different temperatures do **not** accept human error without an explanation do **not** accept pieces of putty not the same unless qualified do **not** accept amount of putty not same do **not** accept systematic / random error	1
(iii)	repeat readings	accept check results again accept do experiment again accept do it again accept compare own results with other groups do **not** accept take more readings	1
total			10

4.2.1.1 Standard circuit diagram symbols

Answer 09 · Mark scheme

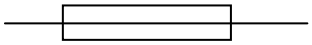
January 2008 | PHY2F | Original Q6 | Legacy

PHY2F

4.2.1.1 Standard circuit diagram symbols

Answer 10 · Mark scheme June 2008 | PHY2F | Original Q3 | Legacy

Question 3

	answers	extra information	mark
(a)(i)	blue		1
(ii)	earth		1
(iii)	rubber / plastic	accept any suitable **named** non conductor eg polypropylene do **not** accept bakelite do **not** accept an insulator	1
(iv)			1
(b)	any **two** from: • draws too high a current • socket overloaded • wiring gets too hot / melts • (may) cause a fire • (may) cause sparking • (possible) physical damage to the socket	accept power for current do **not** accept electricity/ electric for current accept too much current goes through the socket do **not** accept too many currents go through the socket it = socket do **not** accept circuit for socket accept socket for wiring do **not** accept fuse melts or blows do **not** accept plug/ appliances overheating a physical reason, such as stick out from the wall is insufficient ignore reference to electric shocks	2
total			6

4.2.1.1 Standard circuit diagram symbols

Answer 10 · Mark scheme June 2008 | PHY2F | Original Q3 | Legacy

PHY2F


June 08

4.2.1.1 Standard circuit diagram symbols

Answer 11 · Mark scheme

June 2010 | PHY2F | Original Q1 | Legacy

Question 1

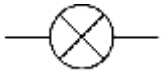question	answers	extra information	mark
1(a)		accept 'the humpback bridge' symbol accept circle with cross but no lines if more than one symbol drawn, no mark unless lamp is labelled	1
1(b)(i)	24	allow **1** mark for correct substitution ie $\frac{2880}{120}$ allow **1** mark for an answer 1440 ignore any unit	2
1(b)(ii)	watt		1
1(c)	larger than	accept correct indication inside the box accept an answer meaning larger than ie greater than	1
Total			**5**

4.2.1.1 Standard circuit diagram symbols

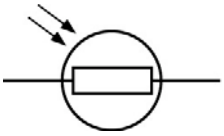
Answer 11 · Mark scheme June 2010 | PHY2F | Original Q1 | Legacy

PHY2F

4.2.1.1 Standard circuit diagram symbols

Answer 12 · Mark scheme June 2012 | PH2FP | Original Q4 | Legacy

Question 4

question	answers	extra information	mark
4(a)(i)	correct symbol ringed 		1
4(a)(ii)	accept any suggestion that would change light intensity, eg: • torch on or off • distance between torch and LDR • lights in room on or off • shadow over the LDR	accept power of torch do **not** accept watts/wattage of torch	1
4(b)	resistance decreases from 600 kΩ to 200 kΩ	 accept by 400 kΩ	1 1
4(c)(i)	no numbers for light intensity **or** light intensity is categoric / a description/not continuous	not enough results is insufficient	1
4(c)(ii)	YES both show that resistance increases with decreasing (light) intensity / brightness	mark is for the reason accept they both get the same results/pattern	 1
4(d)	A circuit that automatically switches outside lights on when it gets dark.		1
Total			**7**

4.2.1.1 Standard circuit diagram symbols

Answer 12 · Mark scheme

June 2012 | PH2FP | Original Q4 | Legacy


PH2FP

4.2.1.1 Standard circuit diagram symbols

Answer 13 · Mark scheme

June 2013 | PH2FP | Original Q3 | Legacy

Question 3

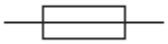question	answers	extra information	mark
3(a)(i)	neutral		1
3(a)(ii)	brown		1
3(b)(i)	centre symbol ringed 	accept any correct indication	1
3(b)(ii)	fuse (wire) melts	accept fuse blows accept fuse breaks / snaps accept burns out appliance doesn't work is insufficient overheat is insufficient do **not** accept blows up	1
3(c)(i)	Toaster (only one with) a metal case / outside	 reason only scores if toaster chosen accept it is metal accept outside / case / metal conducts (electricity) do **not** accept it conducts electricity	1 1
3(c)(ii)	electric shock / electrocution	do **not** accept explosion	1

Question 3 continues on the next page . . .

PH2FP

Question 3 continued . . .

question	answers	extra information	mark
3(d)	overheating of cables **or** fire	it refers to the electric cable accept short circuit / sparking overheating of tape is insufficient do **not** accept electrocution / shock	1
3(e)	stop cable(s) being pulled loose / free and so breaking the circuit **or** and shorting (one wire to another) **or** and causing a fire risk / sparking	accept wire(s) for cable(s) accept to hold cables in place accept appliance / plug would not work	1 1
Total			**10**

4.2.1.1 Standard circuit diagram symbols

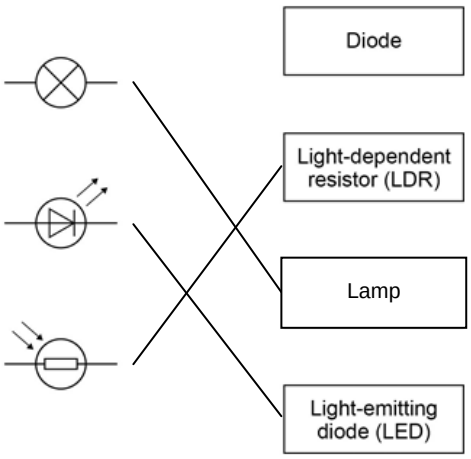
Answer 13 · Mark scheme

June 2013 | PH2FP | Original Q3 | Legacy

PH2FP

4.2.1.1 Standard circuit diagram symbols

Answer 14 · Mark scheme June 2014 | PH2FP | Original Q3 | Legacy

3(a)		allow **1** mark for each correct line if more than one line is drawn from any symbol then all of those lines are wrong	3	AO1 2.3.2
3(b)(i)	half		1	AO1 2.3.2k
3(b)(ii)	3(V)		1	AO2 2.3.2k
3(b)(iii)	V_1		1	AO2 2.3.2k

Question 3 continues on the next page . . .

4.2.1.1 Standard circuit diagram symbols

Question 3 continued . . .

Question	Answers	Extra information	Mark	AO spec ref
3(c)(i)	potential difference / voltage of the power supply	accept the power supply accept the voltage / volts accept number of cells / batteries accept (same) cells / batteries do not accept same ammeter / switch / wires	1	AO3 2.3.2i
3(c)(ii)	bar drawn – height 1.(00)A	ignore width of bar allow **1** mark for bar shorter than 3rd bar	2	AO2 2.3.2i
3(c)(iii)	as the number of resistors increases the current decreases		1	AO3 2.3.2i
Total			**10**	

4.2.1.1 Standard circuit diagram symbols

Answer 14 · Mark scheme

June 2014 | PH2FP | Original Q3 | Legacy

Question	Answers	Extra information	Mark	AO spec ref

Answer 15 · Mark scheme

June 2015 | PH2FP | Original Q7 | Legacy

The full source mark scheme begins on page 135. Follow original question 7 in that document.

4.2.1.1 Standard circuit diagram symbols

Answer 16 · Mark scheme June 2016 | PH2FP | Original Q7 | Legacy

Question	Answers	Extra information	Mark	AO / Spec. Ref.
7(a)	last box ticked 		1	AO1 2.3.2c
7(b)(i)	use hotter water (than 60 °C) **or** add ice cubes	accept use boiling water accept use water at any stated temperature above 60 °C accept add water at any stated temperature below 12 °C use different temperatures is insufficient	1	AO3 2.3.2q
7(b)(ii)	the current increases as the temperature increases		1	AO2 2.3.2q
7(b)(iii)	0.02 (A)		1	AO2 2.3.2q
7(b)(iv)	5 (V) **or** their **(b)(iii)** × 250 correctly calculated	allow **1** mark for correct substitution ie V = 0.02 × 250 **or** V = their **(b)(iii)** × 250	2	AO2 2.3.2h
7(b)(v)	the resistance increases		1	AO3 2.3.2q
Total			**7**	

4.2.1.1 Standard circuit diagram symbols

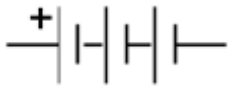
Answer 16 · Mark scheme

June 2016 | PH2FP | Original Q7 | Legacy



4.2.1.1 Standard circuit diagram symbols


Answer 17 · Mark scheme June 2018 | 8463/1F | Original Q3

Question	Answers	Extra information	Mark	AO / Spec. Ref.
03.1	correct circuit symbol 3 cells joined in series in correct orientation eg 	 ignore absence of + symbol	1 1	AO1 4.2.1.1
03.2	$R = \frac{12}{1.6}$ R = 7.5 (Ω)	an answer of 7.5 (Ω) scores **2** marks	 1 1	AO2 4.2.1.3
03.3	4.0 (Ω)	allow their answer to question **03.2** − 3.5 correctly calculated	1	AO2 4.2.2
03.4	it decreases the current would be higher (for the same p.d.) **or** more than one path for charge to flow **or** total resistance is always less than the smallest individual resistance	 reason only scores if correct box is chosen allow current for charge	1 1	AO1 4.2.2
Total			**7**	

4.2.1.1 Standard circuit diagram symbols


Answer 17 · Mark scheme

June 2018 | 8463/1F | Original Q3

 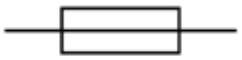

4.2.1.1 Standard circuit diagram symbols


Answer 18 · Mark scheme June 2018 | 8463/1F | Original Q7

Question	Answers	Extra information	Mark	AO / Spec. Ref.
07.1			1	AO1 4.2.1.1
07.2	E = 13 × 230 E = 2990 (J)	an answer 2990 (J) scores **2** marks	1 1	AO2 4.2.4.2
07.3	charge flow = current x time	allow Q = It	1	AO1 4.2.1.2
07.4	1.52 = I × 0.40 $I = \frac{1.52}{0.40}$ I = 3.8 (A)	an answer of 3.8 (A) scores **3** marks	1 1 1	AO2 4.2.1.2
07.5	E = 0.00175 × 205 000 E = 359 (J)	an answer of 359 (J) scores **2** marks allow an answer that rounds to 360 (J) for **2** marks	1 1	AO2 4.3.2.3
Total			**9**	

4.2.1.1 Standard circuit diagram symbols

Answer 18 · Mark scheme

June 2018 | 8463/1F | Original Q7

 

4.2.1.1 Standard circuit diagram symbols

Answer 19 · Mark scheme June 2018 | 8463/1F | Original Q12

Question	Answers	Extra information	Mark	AO/ Spec. Ref
12.1	ammeter and voltmeter symbols correct voltmeter in parallel with wire ammeter in series with wire		1 1 1	AO1 4.2.1.1 4.2.1.3
12.2	**Level 3:** The method would lead to the production of a valid outcome. All key steps are identified and logically sequenced.		5–6	AO1 4.2.1.3
	Level 2: The method would not necessarily lead to a valid outcome. Most steps are identified, but the method is not fully logically sequenced.		3–4	
	Level 1: The method would not lead to a valid outcome. Some relevant steps are identified, but links are not made clear.		1–2	
	No relevant content		0	
	Indicative content • length measured • length varied • current measured • potential difference measured • repeat readings • calculate resistance for each length • resistance = $\frac{\text{potential difference}}{\text{current}}$ • plot a graph of resistance against length • hazard: high current • may cause wire to melt / overheat • may cause burns (to skin) • use low currents			

4.2.1.1 Standard circuit diagram symbols

Answer 19 · Mark scheme

June 2018 | 8463/1F | Original Q12


Question	Answers	Extra information	Mark	AO/ Spec. Ref
12.3	the temperature of the wire would not change		1	AO3 4.2.1.3
12.4	the accuracy of the student's results would be higher the resolution of the length measurement would be higher		1 1	AO3 4.2.1.3
Total			**12**	

4.2.1.1 Standard circuit diagram symbols

Answer 20 · Mark scheme

November 2020 | 8463/1F | Original Q8

Question 8

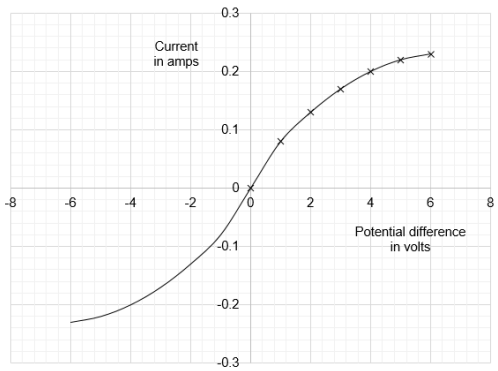Question	Answers	Extra information	Mark	AO / Spec. Ref.
08.1	ammeter and voltmeter symbols correct voltmeter in parallel with lamp ammeter in series with lamp		1 1 1	AO1 4.2.1.1 RPA 4
08.2	smooth curved line of correct shape passing through - 4.0 V, - 0.2 A **or** – 6.0 V, - 0.23 A  	do not accept a line that becomes horizontal 2nd mark conditional on scoring 1st mark	1 1	AO2 4.2.1.4 RPA 4
08.3	potential difference = current × resistance **or** $V = IR$		1	AO1 4.2.1.3 RPA 4
08.4	I = 0.08 (A) 1.0 = 0.08 × R $R = \frac{1.0}{0.08}$ R = 12.5 (Ω)	 allow 1.0 = their I × R provided their I has been obtained from the graph allow $R = \frac{1.0}{\text{their I}}$ allow an answer consistent with their I	1 1 1 1	AO2 4.2.1.3 RPA 4

4.2.1.1 Standard circuit diagram symbols

Answer 20 · Mark scheme

Question	Answers	Extra information	Mark	AO / Spec. Ref.
08.5	ammeter displays a reading when not connected (to a circuit)		1	AO3 4.2.1.4 RPA 4
Total			**11**	

4.2.1.1 Standard circuit diagram symbols

Answer 21 · Mark scheme

June 2022 | 8463/1F | Original Q6

Question 6

Question	Answers	Extra information	Mark	AO / Spec. Ref.
06.1	parallel		1	AO1 4.2.2

Question	Answers	Extra information	Mark	AO / Spec. Ref.
06.2	S_1		1	AO1 4.2.2


Question	Answers	Extra information	Mark	AO / Spec. Ref.
06.3	S_1, S_2 and S_3		1	AO2 4.2.2

Question	Answers	Extra information	Mark	AO / Spec. Ref.
06.4	energy transferred = power × time **or** $E = P \times t$		1	AO1 4.2.4.2

4.2.1.1 Standard circuit diagram symbols

Answer 21 · Mark scheme

Question	Answers	Extra information	Mark	AO / Spec. Ref.
06.5	$3600 = 1200 \times t$ $t = \frac{3600}{1200}$ $t = 3$ (s)		1 1 1	AO2 4.2.4.2

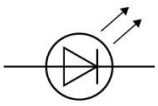Question	Answers	Extra information	Mark	AO / Spec. Ref.
06.6			1	AO1 4.2.1.1

Total Question 6		**8**

4.2.1.1 Standard circuit diagram symbols

Answer 22 · Mark scheme

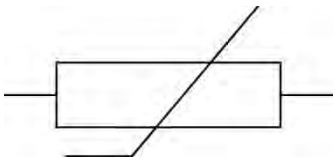
June 2024 | 8463/1F | Original Q2

Question 2

Question	Answers	Extra information	Mark	AO / Spec. Ref.
02.1	50 hertz		1	AO1 4.2.3.1

Question	Answers	Extra information	Mark	AO / Spec. Ref.
02.2	230 volts		1	AO1 4.2.3.1

Question	Answers	Extra information	Mark	AO / Spec. Ref.
02.3	resistance = $\frac{0.45}{0.75}$ resistance = 0.60 (Ω)		1 1	AO2 4.2.1.3

Question	Answers	Extra information	Mark	AO / Spec. Ref.
02.4			1	AO1 4.2.1.1

Question	Answers	Extra information	Mark	AO / Spec. Ref.
02.5	pd across battery - pd across thermistor		1	AO3 4.2.2

4.2.1.1 Standard circuit diagram symbols

Answer 22 · Mark scheme

Question	Answers	Extra information	Mark	AO / Spec. Ref.
02.6	1.5 V (thermistor has the) same resistance as resistor **or** both (components) have a resistance of 200 (Ω)	 MP2 dependent on scoring MP1 allow pd shared equally (between components of equal resistance) allow pd will be half (of the total pd)	1 1	AO3 4.2.2

Question	Answers	Extra information	Mark	AO / Spec. Ref.
02.7	resistance at 15 °C = 200 (Ω) change in resistance = 400 (Ω)	 allow a correct change in resistance from a misread resistance within the range 180 to 220 Ω	1 1	AO2 4.2.1.4

Total Question 2	**10**

4.2.1.1 Standard circuit diagram symbols

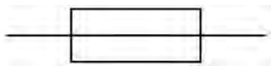
Answer 23 · Mark scheme

June 2024 | 8463/1F | Original Q7

Question 7

Question	Answers	Extra information	Mark	AO / Spec. Ref.
07.1	brown		1	AO1 4.2.3.2

Question	Answers	Extra information	Mark	AO / Spec. Ref.
07.2	blue		1	AO1 4.2.3.2

Question	Answers	Extra information	Mark	AO / Spec. Ref.
07.3			1	AO1 4.2.1.1

Question	Answers	Extra information	Mark	AO / Spec. Ref.
07.4	current = $\frac{2.0}{0.40}$ current = 5.0 (A)		1 1	AO2 4.2.1.2

Question	Answers	Extra information	Mark	AO / Spec. Ref.
07.5	m = 0.000016 (kg) **or** $m = 1.6 \times 10^{-5}$ (kg) $E = 0.000016 \times 60\,000$ E = 0.96 (J)	 allow a correct substitution using an incorrectly / not converted value of m allow an answer consistent with an incorrectly / not converted value of m	1 1 1	AO2 4.3.2.3

4.2.1.1 Standard circuit diagram symbols

Answer 23 · Mark scheme

June 2024 | 8463/1F | Original Q7

Question	Answers	Extra information	Mark	AO / Spec. Ref.
07.6	the total energy will be greater		1	AO3 4.1.2.1 4.3.2.3

Total Question 7	**9**

4.2.1.1 Standard circuit diagram symbols

Answer 24 · Mark scheme

June 2025 | 8463/1F | Original Q5

Question 5

Question	Answers	Extra information	Mark	AO / Spec. Ref.
05.1	(earth wire) green and yellow (live wire) brown (neutral wire) blue		1 1 1	AO1 4.2.3.2

Question	Answers	Extra information	Mark	AO / Spec. Ref.
05.2			1	AO1 4.2.1.1

Question	Answers	Extra information	Mark	AO / Spec. Ref.
05.3	potential difference = $\frac{2420}{11.0}$ potential difference = 220 (V)		1 1	AO2 4.2.4.1

Question	Answers	Extra information	Mark	AO / Spec. Ref.
05.4	resistance = $\frac{2420}{11^2}$ resistance = 20 (Ω)		1 1	AO2 4.2.4.1

Question	Answers	Extra information	Mark	AO / Spec. Ref.
05.5	a greater percentage of energy is usefully transferred by kettle **A** kettle **A** takes less time to boil the same volume of water		1 1	AO3 4.1.1.4 4.1.2.2

Total Question 5	10

4.2.1.1 Standard circuit diagram symbols

ASSESSMENT and QUALIFICATIONS ALLIANCE

Mark scheme June 2003

GCSE

Science: Double Award Co-ordinated

3462

Paper 3F

Copyright © 2003 AQA and its licensors. All rights reserved.

The Assessment and Qualifications Alliance (AQA) is a company limited by guarantee registered in England and Wales 3644723 and a registered charity number 1073334
Registered address: Addleshaw Booth & Co., Sovereign House, PO Box 8, Sovereign Street, Leeds LS1 1HQ
Kathleen Tattersall: *Director General*

4.2.1.1 Standard circuit diagram symbols

INFORMATION FOR EXAMINERS

1. General

The mark scheme for each question shows:

- the marks available for each part of the question;
- the total marks available for the question;
- the typical answer or answers which are expected;
- extra information to help the Examiner make his or her judgement and help to delineate what is acceptable or not worthy of credit or, in discursive answers, to give an overview of the area in which a mark or marks may be awarded.

The extra information is aligned to the appropriate answer in the left-hand part of the mark scheme and should only be applied to that item in the mark scheme.

At the beginning of a part of a question a reminder may be given, for example:
where consequential marking needs to be considered in a calculation;
or the answer may be on the diagram or at a different place on the script.

In general the right hand side of the mark scheme is there to provide those extra details which confuse the main part of the mark scheme yet may be helpful in ensuring that marking is straightforward and consistent.

2. Emboldening

2.1 In a list of acceptable answers where more than one mark is available 'any **two** from' is used, with the number of marks emboldened. Each of the following lines is a potential mark.

2.2 A bold **and** is used to indicate that both parts of the answer are required to award the mark.

2.3 Alternative answers acceptable for a mark are indicated by the use of **or**. (Different terms in the mark scheme are shown by a / ; e.g. allow smooth / free movement.)

3. Marking points

3.1 Marking of Quality of Written Communication

Examiners are reminded of the need to assess QoWC by the following statement appearing in the appropriate parts of the mark scheme:

The answer to this question requires ideas in good English in a sensible order with correct use of scientific terms. Quality of written communication should be considered in crediting points in the mark scheme.

The maximum marks available to a candidate whose answer is not well expressed will be (the number of marks available –1).

3.2 Marking of lists

This applies to questions requiring a set number of responses, but for which candidates have provided extra responses. The general principle to be followed in such a situation is that 'right + wrong = wrong'.

Each error/contradiction negates each correct response. So, if the number of error/contradictions equals or exceeds the number of marks available for the question, no marks can be awarded.

However, responses considered to be neutral (indicated as * in example 1) are not penalised.

Example 1: What is the pH of an acidic solution? (1 mark)

Candidate	Response	Marks awarded
1	4,8	0
2	green, 5	0
3	red*, 5	1
4	red*, 8	0

Example 2: Name two planets in the solar system. (2 marks)

Candidate	Response	Marks awarded
1	Pluto, Mars, Moon	1
2	Pluto, Sun, Mars, Moon	0

3.3 Use of chemical symbols/formulae

If a candidate writes a chemical symbol/formula instead of a required chemical name, full credit can be given if the symbol/formula is correct and if, in the context of the question, such action is appropriate.

3.4 The marking of quantitative relationships

Full credit can be given for a correct quantitative relationship expressed in:

- named units;
- physical quantities;
- standard symbols;
- a combination of physical quantities and units.

No credit can be given for any quantitative relationship expressed in terms of:

- a combination of physical quantities, units and symbols;
- a diagram, e.g. the ohm's law triangle, unless the rest of the answer shows clearly that the candidate understands the relationships involved.

3.5 Marking procedure for calculations

3.5.1 Full marks can be given for a correct numerical answer, as shown in the column 'answers', without any working shown. However, if the answer is incorrect, mark(s) can be gained by correct substitution/working and this is shown in the 'extra information' column.

4.2.1.1 Standard circuit diagram symbols

3.5.2 Where calculations are based on incorrectly recalled relationships, neither the incorrectly recalled relationship, nor the resulting calculation based on the incorrect relationship, will be credited.

3.6 Interpretation of 'it'

Answers using the word 'it' should be given credit only if it is clear that the 'it' refers to the correct subject.

3.7 Errors carried forward

There should be no error carried forward from a previous answer which has been based on wrong science. Any error in the answers to a structured question should be penalised once only.

Examples

(a) A candidate who calculates average speed using speed = time/distance **and** then proceeds to use this incorrect answer to calculate an acceleration based on the correct quantitative relationship should be given credit for the use of the correct acceleration relationship but none for either numerical answer.

(b) A candidate who incorrectly calculates average speed using speed = distance/time and then proceeds to use this incorrect value to calculate an acceleration based on the correct quantitative relationship, should be given credit for the use of both correct quantitative relationships **and** for the correct substitution and use of the incorrect value in the calculation of the rate of acceleration.

Papers should be constructed in such a way that the number of times errors can be carried forward are kept to a minimum. Allowances for errors carried forward are most likely to be restricted to calculation questions and should be shown by the abbreviation e.c.f. in the marking scheme.

3.8 Phonetic spelling

The phonetic spelling of correct scientific terminology should be credited **unless** there is a possible confusion with another technical term.

3.9 Brackets

(…..) is used to indicate information which is not essential for the mark to be awarded but is included to help the examiner identify the sense of the answer required.




3.10 Unexpected Correct Answers not in the Mark Scheme

The Examiner should use professional judgement to award credit where a candidate has given an unexpected correct answer which is not covered by the mark scheme. The Examiner should consult with the Team Leader to confirm the judgement. The Team Leader should pass this answer on to the Principal Examiner with a view to informing all examiners.

4.2.1.1 Standard circuit diagram symbols

Double Award
Foundation Tier 3462/3F

3462/3F Q1

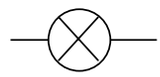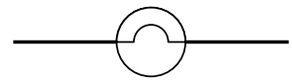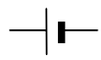question	answers	extra information	mark
(a)	circuit symbol for a lamp correct 	accept  accept any standard of drawing providing circuit would work	1
	circuit symbol for a cell correct 		1
	2 lamps drawn in parallel with 3 cells	polarity of cells must be correct (+ to –) but cells may be either way around	1
(b)	4.5		1
(c)	the same as	accept any clear indication of the correct answer	1
total			5

4.2.1.1 Standard circuit diagram symbols

3462/3F Q2

question	answers	extra information	mark
(a)	gas		1
(b)	fuel burning stations produce electricity at any time / all the time wind generator can only produce when the wind is strong enough	accept fuel available all the time accept it's not always windy	1 1
(c)	no fuel is burnt **or** no fuel is used **or** uses only energy from wind **or** does not emit harmful gases / soot / smoke	do **not** accept wind is natural / environmentally friendly / renewable answer must be in terms of wind, **not** negative of fuel burning specific examples of gases CO_2, SO_2, acid rain and greenhouse gases can be accepted ozone negates credit	1
total			4

4.2.1.1 Standard circuit diagram symbols

3462/3F Q3

question	answers	extra information	mark
(a)(i)	microwaves		1
(ii)	infra red		1
(iii)	ultrasonic		1
(b)(i)	B		1
(ii)	A		1
(c)	disturbance / vibration / movement direction	accept motion / force do **not** accept energy	1 1
(d)	sound wave	accept any clear indication of the correct answer	1
total			8

4.2.1.1 Standard circuit diagram symbols

3462/3F Q4

question	answers	extra information	mark
(a)(i)	heat		1
(ii)	temperature increases **or** (cause) convection (currents)	accept gets warmer accept gets hotter	1
(iii)	60% **or** 0.6	60 without % scores **1** mark 0.6 with a unit scores **1** mark 60 with incorrect unit scores **1** mark **or** correct substitution $\frac{120}{200}$ for **1** mark	2
(b)	street more (energy transferred as) light **or** less (energy transferred as) heat **or** useful energy output the highest	 can only score this mark if first mark scored all efficiencies calculated correctly score 2nd mark point	1 1
total			6


4.2.1.1 Standard circuit diagram symbols

3462/3F Q5

question	answers	extra information	mark
(a)	MN	accept 5.8, 8 seconds must include unit	1
(b)	LM	accept 0.8, 5.8 seconds must include unit	1
(c)(i)	0.8		1
(ii)	drinking alcohol		1
(d)	straight (by eye) line starting at 0.8 seconds line drawn steeper than LM starting before L	 ignore lines going beyond 2 seconds but line must exceed 2.5 metres per second before terminating	1 1
total			6


4.2.1.1 Standard circuit diagram symbols

3462/3F Q6

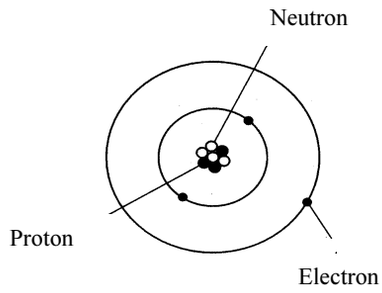question	answers	extra information	mark
(a)(i)	each correct label scores 1 mark  		3
(ii)	neutron		1
(iii)	7 number of protons and neutrons **or** number of nucleons **or** number of particles in the nucleus	 accept number of particles in the centre only if first answer = 7	1 1
(b)(i)	50 ± 5		1
(ii)	50 ± 5	accept their (b)(i)	1
(iii)	less	accept any way of indicating the correct answer	1
total			9

4.2.1.1 Standard circuit diagram symbols

3462/3F Q7

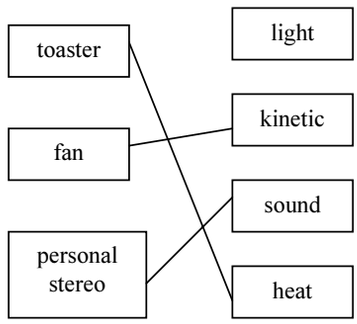question	answers	extra information	mark
(a)	each correct line scores 1 mark  	if more than 3 lines are drawn mark incorrect ones first, to a maximum of 3 lines	3
(b)	toaster	accept 1.2 kW	1
(c)(i)	400		1
(ii)	£24 **or** 2400p	full credit for their (c)(i) × 6p for full credit the correct numerical answer must have the correct unit an answer of 24 or 2400 with no unit or the incorrect unit scores **1** mark (c)(i) × 6 incorrectly evaluated scores **1** mark	2
(d)	6	allow 6000 for **1** mark allow 3 × 2 for **1** mark	2
total			9

4.2.1.1 Standard circuit diagram symbols

3462/3F Q8

question	answers	extra information	mark
(a)(i)	friction	accept any way of indicating the correct answer	1
(ii)	gravity	accept any way of indicating the correct answer	1
(b)(i)	accelerates **or** speed / velocity increases	accept faster and faster (**1** mark) do **not** accept faster pace / falls faster or suggestions of a greater but constant speed	1
	downwards / falls	accept towards the Earth / ground this may score in part (b)(ii) if it does not score here and there is no contradiction between the two parts	1
(ii)	constant speed / velocity **or** terminal velocity / speed **or** zero acceleration	stays in the same place negates credit	1
total			5

4.2.1.1 Standard circuit diagram symbols

3462/3F Q9

question	answers	extra information	mark
(a)(i)	X – mantle		1
	Y – inner core	do **not** accept solid core	1
(ii)	different to the crust **or** contains a lot of (heavy) metals	accept iron and nickel for metals	1
	higher (average) density **or** denser	density higher than 5500 (kg/m^3) gets **2** marks	1
(b)	animals were able to move from one continent to the other		1
	(when bridge broke) animals evolved differently	accept animals adapted differently	1
(c)(i)	earthquakes occur at the boundary between plates **or** earthquakes occur where plates push against each other		1
	there are no plate boundaries running through Britain	accept Britain is not near the edge of a plate	1
(ii)	convection currents (in the mantle) **or** heat released by (natural) radioactive processes		1
total			9

4.2.1.1 Standard circuit diagram symbols

3462/3F Q10

question	answers	extra information	mark
(a)(i)	outside the Earth **or** not from the Earth	accept alien accept life from / on another planet / space accept our planet for Earth	1
(ii)	radio telescope(s)	do **not** accept telescopes do **not** accept satellite dishes do **not** accept radio receivers **or** transmitters	1
(b)(i)	galaxies	do **not** accept stars	1
(ii)	any **one** from: the pulses were regular pulses from space are usually random (scientists) thought technology had been used to produce the pulses neutron stars were unknown signals from a single point	 accept signals / beats for pulses accept noise for random pulses idea of regular but not continuous	1
(iii)	neutron star is (the matter / mass) left behind after a star / red giant explodes (as a super nova)	 accept after a super nova (explosion) neutron star causing super nova gets no credit	1 1
(c)(i)	carried on the balloon / equipment	accept carried by a rocket / aircraft / satellite birds negates credit	1
(ii)	on comets or meteors	accept meteorites / shooting stars accept returning space craft accept solar wind ignore asteroids accept ufo do **not** accept solar flares do **not** accept satellites	1
total			8

4.2.1.1 Standard circuit diagram symbols

3462/3F Q11

question	answers	extra information	mark
(a)	silver is a (good) reflector of <u>heat</u> (radiation) **or** silver reflects the heat (radiation)	fact heat = infra red ignore references to light accept shiny for silver good radiator negates the mark ignore references to good conductor do **not** accept bounce back	1
	less heat is lost through the board **or** more heat is retained by the shirt	explanation accept both sides of shirt heated reflects heat back up gets **1** mark only ignore mention of friction	1
(b)	metal soleplate	accept soleplate / bottom / metal do **not** accept outside / case	1
(c)	plastic **or** rubber	accept any named plastic do **not** accept wood	1
	it is a (good) insulator **or** it is a poor conductor	ignore mention of heat if in conjunction with electricity	1
(d)	**Quality of written communication** *The answer to this question requires ideas in good English in a sensible order with correct use of scientific terms. Quality of written communication should be considered in crediting points in the mark scheme.*	*Maximum of **2** marks if ideas not well expressed.*	
	pulls iron bolt down **or** attracts the iron bolt **or** moves bolt out of plunger	answers in terms of charges attracting or repelling gain no credit	1
	plunger pushed / moved to the right (by spring) **or** plunger released		1
	push switch opens / goes to off / goes to right	accept circuit is broken for maximum credit the points must follow a logical sequence 3 correct points but incorrect sequence scores **2** marks only ignore reset action	1
total			8


4.2.1.1 Standard circuit diagram symbols

3462/3F Q12

question	answers	extra information	mark
(a)(i)	any **one** from:		1
	the ground	do **not** accept mobile phones	
	the air		
	radon (gas)		
	building materials		
	buildings		
	rocks / granite		
	food		
	cosmic rays **or** solar rays	accept from outer space accept sun but **not** sunlight	
	X-rays	accept medical uses	
	nuclear weapons testing		
	nuclear power stations / accidents		
(ii)	2	allow $\frac{1200}{60\times10}$ **or** $\frac{1200}{600}$ **or** 120 for **1** mark	2
(b)		answers must be comparative accept converse answers throughout	
	alpha: the count rate is (greatly) reduced by the card **or** the card absorbs alphas but not betas	accept paper for the card	1
	beta: the count rate is (greatly) reduced by the metal **or** the thin metal absorbs alphas and betas **or** the thin metal absorbs all of the radiation (from the source)	accept aluminium for the metal	1
	gamma: would pass through the thin metal but count rate is background **or** no radiation passing through **or** a higher reading would be recorded **or** to reduce the count to 2 would require much more than 3 mm of metal	accept aluminium for the metal accept lead / aluminium for the metal	1
total			6

4.2.1.1 Standard circuit diagram symbols

3462/3F Q13

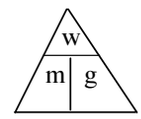question	answers	extra information	mark
(a)(i)	weight = mass × g.f.s.	accept w = m × g accept gravity for gfs accept  provided subsequent use of Δ correct do **not** accept N = kg × N/kg	1
(ii)	675	75 × 9 for **1** mark	2
(iii)	g.(f.s.) is higher (on Earth than Venus)	accept gravity for g.f.s. do **not** accept g.f.s. is lower unless answer states on Venus	1
(iv)	orbit time for Jupiter is <u>longer</u> / longest (than for the other planets)	do **not** give any credit for an answer that includes a comparison of diameter **or** a comparison of g.f.s.	1
(b)	**Quality of written communication** *The answer to this question requires ideas in good English in a sensible order with correct use of scientific terms. Quality of written communication should be considered in crediting points in the mark scheme.* any **two** from: dust <u>and</u> gas **or** remnants of a super nova pulled together by (force of) <u>gravity</u> nuclear fusion starts	*Maximum of **1** mark if ideas not well expressed.* accept hydrogen for dust and gas do **not** accept hydrogen burns although candidates may include more detail these points are essential to score the credit	2
total			7

GCSE 2004
June Series

ASSESSMENT and QUALIFICATIONS ALLIANCE

Mark Scheme

Physics Specification B
3451/F

Mark schemes are prepared by the Principal Examiner and considered, together with the relevant questions, by a panel of subject teachers. This mark scheme includes any amendments made at the standardisation meeting attended by all examiners and is the scheme which was used by them in this examination. The standardisation meeting ensures that the mark scheme covers the candidates' responses to questions and that every examiner understands and applies it in the same correct way. As preparation for the standardisation meeting each examiner analyses a number of candidates' scripts: alternative answers not already covered by the mark scheme are discussed at the meeting and legislated for. If, after this meeting, examiners encounter unusual answers which have not been discussed at the meeting they are required to refer these to the Principal Examiner.

It must be stressed that a mark scheme is a working document, in many cases further developed and expanded on the basis of candidates' reactions to a particular paper. Assumptions about future mark schemes on the basis of one year's document should be avoided; whilst the guiding principles of assessment remain constant, details will change, depending on the content of a particular examination paper.

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols

Further copies of this Mark Scheme are available from:

Publications Department, Aldon House, 39, Heald Grove, Rusholme, Manchester, M14 4NA
Tel: 0161 953 1170

or

download from the AQA website: www.aqa.org.uk

Copyright © 2004 AQA and its licensors

COPYRIGHT
AQA retains the copyright on all its publications. However, registered centres for AQA are permitted to copy material from this booklet for their own internal use, with the following important exception: AQA cannot give permission to centres to photocopy any material that is acknowledged to a third party even for internal use within the centre.

Set and published by the Assessment and Qualifications Alliance.

The Assessment and Qualifications Alliance (AQA) is a company limited by guarantee registered in England and Wales 3644723 and a registered charity number 1073334. Registered address AQA, Devas Street, Manchester. M15 6EX. *Dr Michael Cresswell Director General*

4.2.1.1 Standard circuit diagram symbols

GCSE PHYSICS

INFORMATION FOR EXAMINERS

1. General

The mark scheme for each question shows:

- the marks available for each part of the question;
- the total marks available for the question;
- the typical answer or answers which are expected;
- extra information to help the Examiner make his or her judgement and help to delineate what is acceptable or not worthy of credit or, in discursive answers, to give an overview of the area in which a mark or marks may be awarded.

The extra information is aligned to the appropriate answer in the left-hand part of the mark scheme and should only be applied to that item in the mark scheme.

At the beginning of a part of a question a reminder may be given, for example:
where consequential marking needs to be considered in a calculation;
or the answer may be on the diagram or at a different place on the script.

In general the right hand side of the mark scheme is there to provide those extra details which confuse the main part of the mark scheme yet may be helpful in ensuring that marking is straightforward and consistent.

2. Emboldening

2.1 In a list of acceptable answers where more than one mark is available 'any **two** from' is used, with the number of marks emboldened. Each of the following lines is a potential mark.

2.2 A bold **and** is used to indicate that both parts of the answer are required to award the mark.

2.3 Alternative answers acceptable for a mark are indicated by the use of **or**. (Different terms in the mark scheme are shown by a / ; e.g. allow smooth / free movement.)

3. Marking points

3.1 Marking of Quality of Written Communication

Where *Quality of written communication* appears in the mark scheme, one mark is to be awarded for either of the following points:

- Using correct scientific terms
- Correct sequencing or linking of ideas or points

The mark scheme will specify which of the points is to be awarded in a particular question. A QoWC mark can be awarded for a scientific answer, even if it is not accurate. It cannot be awarded for a nonsensical or non-scientific answer.
On the script, the QoWC tick should be identified by a 'q' written next to it.

3.2 Marking of lists

This applies to questions requiring a set number of responses, but for which candidates have provided extra responses. The general principle to be followed in such a situation is that 'right + wrong = wrong'.

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols

Each error/contradiction negates each correct response. So, if the number of error/contradictions equals or exceeds the number of marks available for the question, no marks can be awarded.

However, responses considered to be neutral (indicated as * in example 1) are not penalised.

Example 1: What is the pH of an acidic solution? (1 mark)

Candidate	Response	Marks awarded
1	4,8	0
2	green, 5	0
3	red*, 5	1
4	red*, 8	0

Example 2: Name two planets in the solar system. (2 marks)

Candidate	Response	Marks awarded
1	Pluto, Mars, Moon	1
2	Pluto, Sun, Mars, Moon	0

3.3 Use of chemical symbols/formulae

If a candidate writes a chemical symbol/formula instead of a required chemical name, full credit can be given if the symbol/formula is correct and if, in the context of the question, such action is appropriate.

3.4 The marking of quantitative relationships

Full credit can be given for a correct quantitative relationship expressed in:

- named units;
- physical quantities;
- standard symbols;
- a combination of physical quantities and units.

No credit can be given for any quantitative relationship expressed in terms of:

- a combination of physical quantities, units and symbols;
- a diagram, e.g. the ohm's law triangle, unless the rest of the answer shows clearly that the candidate understands the relationships involved.

3.5 Marking procedure for calculations

3.5.1 Full marks can be given for a correct numerical answer, as shown in the column 'answers', without any working shown.
However:

- if the answer is incorrect, mark(s) can be gained by correct substitution/working and this is shown in the 'extra information' column;
- if the answer is correct, but an incorrect relationship is written in the working, then no marks can be awarded (see 3.5.2).

3.5.2 Where calculations are based on incorrectly recalled relationships, neither the incorrectly recalled relationship, nor the resulting calculation based on the incorrect relationship, will be credited.

3.6 Interpretation of 'it'

Answers using the word 'it' should be given credit only if it is clear that the 'it' refers to the correct subject.

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols

3.7 Errors carried forward

There should be no error carried forward from a previous answer which has been based on wrong science. Any error in the answers to a structured question should be penalised once only.

Examples

(a) A candidate who calculates average speed using speed = time/distance **and** then proceeds to use this incorrect answer to calculate an acceleration based on the correct quantitative relationship should be given credit for the use of the correct acceleration relationship but none for either numerical answer.

(b) A candidate who incorrectly calculates average speed using speed = distance/time and then proceeds to use this incorrect value to calculate an acceleration based on the correct quantitative relationship, should be given credit for the use of both correct quantitative relationships **and** for the correct substitution and use of the incorrect value in the calculation of the rate of acceleration.

Papers should be constructed in such a way that the number of times errors can be carried forward are kept to a minimum. Allowances for errors carried forward are most likely to be restricted to calculation questions and should be shown by the abbreviation e.c.f. in the marking scheme.

3.8 Phonetic spelling

The phonetic spelling of correct scientific terminology should be credited **unless** there is a possible confusion with another technical term.

3.9 Brackets

(…..) is used to indicate information which is not essential for the mark to be awarded but is included to help the examiner identify the sense of the answer required.

3.10 Interpretation of marginal points

There will be times when the answer is almost, but not quite, correct. Some examiners would award a mark while others would not. In any one script, an attempt should be made to balance these nearly correct answers by giving the mark on some occasions but not on others. If this is not done, the marking would end up being too lenient or too harsh.

3.11 Unexpected Correct Answers not in the Mark Scheme

The Examiner should use professional judgement to award credit where a candidate has given an unexpected correct answer which is not covered by the mark scheme. The Examiner should consult with the Team Leader to confirm the judgement. The Team Leader should pass this answer on to the Principal Examiner with a view to informing all examiners.

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols

GCSE Physics
Foundation Tier 3451/F

3451F Q1

question	answers	extra information	mark
(a)	comet	correct order only	1
	elliptical		1
	Milky Way		1
	Universe		1
(b)(i)	D A C B	allow **2** marks for two letters in the correct place allow **1** mark for one letter in the correct place	3
(ii)	A		1
total			8

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols


3451F Q2

question	answers	extra information	mark
(a)	95		1
(b)	alpha	accept correct symbol	1
(c)	any **two** from: • radiation is outside the body • radiation will not reach (living) cells • radiation absorbed by the air	 accept detector is on ceiling or high up the wall accept radiation cannot pass through the body / skin accept cannot pass through the plastic casing do **not** accept because it is alpha radiation – unless qualified do **not** accept does not give off harmful substance do **not** accept cannot pass through building materials etc.	2
(d)	less (than)		1
total			5

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols

3451F Q3

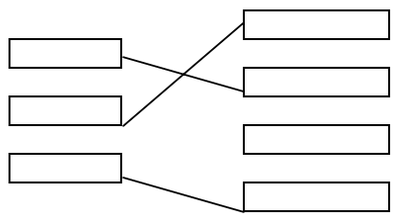question	answers	extra information	mark
(a)	generator	accept dynamo accept alternator	1
(b)(i)	1400	ignore units	1
(ii)	0.3 or 30%	any incorrect unit penalise **1** mark allow **1** mark for the correct use of 600 **or** 0.3% **or** 30	2
(c)	**1** mark for each correct link 	if more than 3 lines are drawn, mark only 3 lines starting with those that are incorrect	3
(d)(i)	110	no tolerance	1
(ii)	12	no tolerance	1
(iii)	wind speed may be too low to operate the generator	accept wind may not always blow accept power depends on wind speed accept does not generate if wind speed is too high accept does not generate if wind speed is above 12 (m/s) accept does not generate if wind speed is below 1.6 (m/s) accept it is unreliable do **not** accept answers referring to cost only	1
total			10

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols

3451F Q4

question	answers	extra information	mark
(a)	B E A D	allow **1** mark for each letter in the correct place, to a maximum of **3** marks	3
(b)	(a spark) may cause the (petrol vapour) to explode / ignite connect tanker to earth with a (conducting) wire / chain **or** earth the tanker	accept petrol for (petrol vapour) accept catch fire for explode accept ground for earth	1 1
(c)	**Quality of written communication** any **two** from: • when current greater than fuse rating / value • fuse (becomes hot and) melts / burns out • circuit is broken	for a logical sequence accept when current too great for appliance do **not** accept 'if there is too much current' do **not** accept voltage or electricity accept fuse blows / breaks accept circuit switched off this cannot score credit on its own	1 2
total			8

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols

3451F Q5

question	answers	extra information	mark
(a)(i)	crust		1
(ii)	inner core is <u>solid</u> outer core is liquid	do **not** accept just rock inner core is denser / hotter than outer core gets **2** marks accept one is solid and one is liquid for **1** mark accept they are different densities for **1** mark wrong way round = **0** marks	1 1
(b)	seismograph		1
(c)	difficult to measure (slow) movement (1) of plates (1) dependent mark **or** difficult to measure friction / forces (1) between plates (1) dependent mark		1 1
(d)	geothermal		1
(e)(i)	5000		1
(ii)	2500		1
total			9

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols


3451F Q6

	answers	extra information	mark
(a)	converging image object image object shorter		1 1 1 1 1 1
(b)(i)	(Earth's) gravity	accept centripetal accept minor misspellings, however, do **not** credit any response which could be 'centrifugal'	1
(ii)	to(wards) (the centre of the) Earth	allow inwards do **not** accept downwards	1
(c)(i)	**either** friction (force) **or** centripetal force between the tyres / wheels and (the surface of) the road	 allow grip allow on the tyres / wheels **or** towards the centre of the bend / arc / circle	 1 1
(ii)	mass **or** speed **or** momentum radius / diameter	allow weight allow velocity do **not** credit 'curvature' or 'circumference'	1 1
(d)	centripetal	accept minor misspellings (see above)	1
total			13

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols

3451F Q7

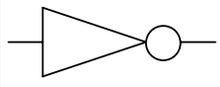	answers	extra information	mark
(a)(i)	two switches in series **and** circuit complete	ignore small imperfections	1
(ii)	two switches in parallel **and** circuit complete	ignore small imperfections	1
(iii)	one switch in parallel with the cell / lamp (but **not** both)	ignore small imperfections	1
(iv)	(i) AND (ii) OR (iii) NOT	accept 'and' accept 'or' accept 'not'	1 1 1
(b)(i)	when it is light the sensor sends on / high / 1 signal to the gate off / low / 0 sent to the lamp **or** when it is dark the sensor sends off / low / 0 signal to the gate (1) on / high / 1 sent to the lamp (1)		1 1
(ii)	any suitable application	e.g. to switch a security light on (and off) e.g. to switch a light on when it is dark do **not** credit just '… to switch a light on / off'	1
(c)(i)		accept shading-in of either or both parts end connections are not required accept any orientation	1
(ii)	1 0 **or** 0 1 0 1 1 0	all correct	1
(iii)	truth (table)		1
total			12

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols


3451F Q8

question	answers	extra information	mark
(a)	60		1
(b)	$5\frac{1}{2}$ hours	must include unit	1
(c)	30		1
(d)	30 minutes or $\frac{1}{2}$ hour	must include unit	1
(e)	D **and** E least steep part of the graph	accept finish for E accept correct numbers from axes with units accept covers smallest distance in a set time accept only moves 5 km in $1\frac{1}{2}$ hours (accept anything between 5 and 6) ignore horse is tired	1 1
total			6

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols


3451F Q9

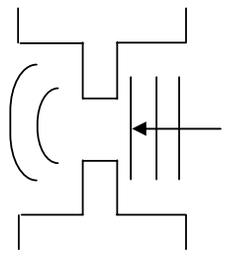question	answers	extra information	mark
(a)(i)	any **one** from: • (doctors) to see inside a patients body **or** endoscope • telephone cables • optical fibre / fibre optic lamps **or** (artificial) Christmas trees • data transfer **or** internet connection	 accept keyhole surgery do **not** accept flex **or** wires for cable accept decorative / ornamental lighting accept any feasible practical suggestion for taking light to a difficult to access place do **not** accept lighting unqualified do **not** accept lamp unqualified do **not** accept communications unless clarified	1
(ii)	(incident) ray angle greater than critical angle total internal reflection occurs	either order accept (incident) ray greater than 42° accept TIR do **not** accept just description of TIR	1 1
(b)(i)	waves shown diffracting in the correct direction 	ignore wavelength	1
(ii)	diffraction	accept diffract / diffracted	1
total			5

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols

3451F Q10

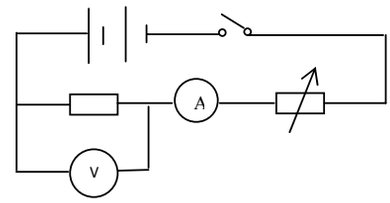question	answers	extra information	mark
(a)	all symbols correct	 accept push switch symbol switch may be open or closed any lines through symbols = **0** marks	1
	correct circuit drawn voltmeter must be across resistor only	polarity of cells not relevant provided they are joined correctly two cells are required in the diagram ignore the order of the components allow small gaps in circuit omission of any component = **0** marks	1
(b)(i)	potential difference = current × resistance	accept voltage or p.d. for potential difference accept $V = I \times R$ accept  provided subsequent use correct do **not** accept C for current	1
(ii)	2	allow **1** mark for correct substitution wrong working loses both marks	2
(iii)	straight line drawn <u>through the origin</u> straight line passes through $I = 0.4, V =$ their (b)(ii) / 2 **and** 0.0	judge by eye this mark may be awarded if all points shown including these points are correct even if no line is drawn N.B. a curve scores **0** marks	1 1 dep
(c)	temperature <u>increases</u>	accept filament lamp / it gets <u>hotter</u> allow heat for temperature	1
total			8

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols

3451F Q11

question	answers	extra information	mark
(a)(i)	gamma rays	accept gamma accept correct symbol	1
(ii)	infra red	accept IR	1
(b)	ultraviolet <u>absorbed</u> by ink (energy) given out as light	 accept glows / luminous accept for **both** marks the ink is fluorescent do **not** accept answers in terms of uv being reflected	1 1
(c)	any **two** from: • UV can damage / kill / ionise / alter (normal) cells • change DNA structure **or** mutate • (normal) cells may become cancerous	 do **not** accept attacks cells **or** burns skin accept may cause (skin) cancer accept abnormal cell multiplication	2
(d)(i)	microwaves **and** infra red	both answers needed in either order do **not** accept heat for IR	1
(ii)	0.9	 allow **1** mark for the <u>correct</u> use of 1.8 (kW) ($1.8 \times \frac{1}{2}$ or 1.8×30) i.e. adding the correct 2 power values	2
total			9

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols


3451F Q12

question	answers	extra information	mark
(a)(i)	accelerating	accept getting faster accept speed / velocity increasing	1
(ii)	acceleration <u>increases</u>	accept velocity / speed increases <u>more</u> rapidly do **not** accept velocity / speed increases	1
(b)(i)	$\text{acceleration} = \frac{\text{change in velocity}}{\text{time (taken)}}$	accept $a = \frac{v - u}{t}$ **or** $a = \frac{v_1 - v_2}{t}$ do **not** accept velocity for change in velocity do **not** accept change in speed do **not** accept $a = \frac{v}{t}$	1
(ii)	15	allow **1** mark for an answer of 900 **or** for <u>correct</u> use of 540 seconds	2
(iii)	velocity includes direction	accept velocity is a vector (quantity) accept converse answer	1
(c)	force of gravity (between <u>shuttle</u> and Earth) plus correct orbital speed (makes <u>shuttle</u> move in a curve)	accept gravitational pull if used correctly accept forward motion **or** constant speed for orbital speed accept it is travelling fast enough accept for **2** marks the force of gravity provides the <u>centripetal</u> force	1 1
(d)	black is a good emitter of radiation **or** to limit the temperature rise inside the shuttle	accept heat for radiation accept the tiles are good insulation do **not** accept black absorbs heat on its own do **not** accept tiles are heat proof	1
total			9

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols

3451F Q13

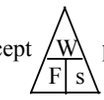question	answers	extra information	mark
(a)(i)	work (done) = force (applied) × distance (moved)	accept W = F × s or W = F × d accept  provided subsequent method is correct	1
(ii)	240 000 joules	allow **1** mark for correct substitution **or** correct use of 1200 (N) accept J do **not** accept j / Nm	2 1
(b)	800 (watts)	accept 0.8 kW accept their (a)(ii) ÷ 300 correctly evaluated for **2** marks allow **1** mark for correct substitution (a)(ii) ÷ 5 correctly evaluated for **1** mark	2
(c)(i)	any **one** from: • needs to raise the chair / lift • lifting more than one chair • energy transfer to the surroundings correctly qualified	 allow lifting more than 2 people implication of a heavier weight accept loss for transfer do **not** accept motor inefficient do **not** accept motor gets hot do **not** accept friction unless the location is specified as external to the motor	1
(ii)	electrical potential	accept electric **both** answers required for the mark	1
total			8

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols

3451F Q14

	answers	extra information	mark
(a)(i)	current		1
(ii)	resistance decreases	 accept 'the flow of electrons / current (through it) increases' for **1** mark do **not** credit just '… it will get warmer'	1 1
(b)	input sensor → controlled by the processor processor → detects changes in the environment output device → decides what action is needed	all pairs correct one pair correct for **1** mark	2
(c)(i)	potential divider	accept voltage divider	1
(ii)	4 (volts)	$6 \times \frac{30}{45}$ for **1** mark	2
(iii)	across the new resistor…(will) increase across R_2 … (will) decrease	 N.B. independent marks	1 1
total			10

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols

3451F Q15

	answers	extra information	mark
(a)	relay (normally open) (switch)	each mark is independent	1
	… switch on a (larger) current (in another circuit) **or** switch on a higher voltage circuit	do **not** accept switch on another circuit **or** smaller / equal current	1
	light emitting diode / LED	do **not** credit LDR	1
	… in one / direct / certain direction **or** from left to right	**or** when the cathode is connected to the negative terminal / side **or** when the left-hand side is connected to the positive terminal / side do **not** credit just '… is big enough' do **not** accept 'positive direction'	1
	AND gate	accept 'and' gate do **not** accept numerical values unless expanded	1
	… (both) inputs are on / high / 1 **or** current flows in both inputs		1
(b)	**Quality of written communication**	If in a sensible order which clearly indicates advantages or disadvantages, including answers in the form of a table **or** as bullet points Q ✓ Q X	1
	any **three** from: • advantage of mobile phones • drawback of mobile phones • benefit of the Internet • drawback of the Internet	 e.g. more convenient for service engineers e.g. calls can be received away from base e.g. privacy can be more easily invaded e.g. drivers can be distracted e.g. microwaves / radio waves can / may cause damage to the brain e.g. access to educational material e.g. some material is salacious e.g. spam (on external e-mail) these are examples candidates may be credited for a variety of responses	3
total			10

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols

3451F Q16

question	answers	extra information	mark
(a)	**Y** and **Z**		1
	they have the same number of protons **or** same atomic number	accept they have the same number of electrons **or** same number of protons **and** electrons allow only different in number of neutrons N.B. independent marks	1
(b)	**Quality of written communication**	for correct use of terms underlined in B **or** C Q ✓ Q X	1
	A – alpha particle passes straight through the empty space of the atom **or** it is a long way from the nucleus B – alpha particle <u>deflected</u> / <u>repelled</u> / <u>repulsed</u> by the (positive) <u>nucleus</u> C – alpha particle heading straight for the <u>nucleus</u> is <u>deflected</u> / <u>repelled</u> / <u>repulsed</u> backwards	describes 3 tracks correctly for **2** marks describes 2 or 1 track correctly for **1** mark do **not** accept hits the nucleus do **not** accept answers referring to refraction do **not** accept answers in terms of reflected backwards unless qualified in terms of repulsion mention of difference in charge on nucleus negates that track	max 2
total			5

Copyright © 2004 AQA and its licensors

GCSE 2004
June Series

ASSESSMENT and QUALIFICATIONS ALLIANCE

Mark Scheme

Science: Double Award
Specification B (Co-ordinated)
3462/3F

Mark schemes are prepared by the Principal Examiner and considered, together with the relevant questions, by a panel of subject teachers. This mark scheme includes any amendments made at the standardisation meeting attended by all examiners and is the scheme which was used by them in this examination. The standardisation meeting ensures that the mark scheme covers the candidates' responses to questions and that every examiner understands and applies it in the same correct way. As preparation for the standardisation meeting each examiner analyses a number of candidates' scripts: alternative answers not already covered by the mark scheme are discussed at the meeting and legislated for. If, after this meeting, examiners encounter unusual answers which have not been discussed at the meeting they are required to refer these to the Principal Examiner.

It must be stressed that a mark scheme is a working document, in many cases further developed and expanded on the basis of candidates' reactions to a particular paper. Assumptions about future mark schemes on the basis of one year's document should be avoided; whilst the guiding principles of assessment remain constant, details will change, depending on the content of a particular examination paper.

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols

Further copies of this Mark Scheme are available from:

Publications Department, Aldon House, 39, Heald Grove, Rusholme, Manchester, M14 4NA
Tel: 0161 953 1170

or

download from the AQA website: www.aqa.org.uk

Copyright © 2004 AQA and its licensors

COPYRIGHT
AQA retains the copyright on all its publications. However, registered centres for AQA are permitted to copy material from this booklet for their own internal use, with the following important exception: AQA cannot give permission to centres to photocopy any material that is acknowledged to a third party even for internal use within the centre.

Set and published by the Assessment and Qualifications Alliance.

The Assessment and Qualifications Alliance (AQA) is a company limited by guarantee registered in England and Wales 3644723 and a registered charity number 1073334. Registered address AQA, Devas Street, Manchester. M15 6EX. *Dr Michael Cresswell Director General*

4.2.1.1 Standard circuit diagram symbols

SCIENCE: DOUBLE AWARD CO-ORDINATED

INFORMATION FOR EXAMINERS

1. General

The mark scheme for each question shows:

- the marks available for each part of the question;
- the total marks available for the question;
- the typical answer or answers which are expected;
- extra information to help the Examiner make his or her judgement and help to delineate what is acceptable or not worthy of credit or, in discursive answers, to give an overview of the area in which a mark or marks may be awarded.

The extra information is aligned to the appropriate answer in the left-hand part of the mark scheme and should only be applied to that item in the mark scheme.

At the beginning of a part of a question a reminder may be given, for example:
where consequential marking needs to be considered in a calculation;
or the answer may be on the diagram or at a different place on the script.

In general the right hand side of the mark scheme is there to provide those extra details which confuse the main part of the mark scheme yet may be helpful in ensuring that marking is straightforward and consistent.

2. Emboldening

2.1 In a list of acceptable answers where more than one mark is available 'any **two** from' is used, with the number of marks emboldened. Each of the following lines is a potential mark.

2.2 A bold **and** is used to indicate that both parts of the answer are required to award the mark.

2.3 Alternative answers acceptable for a mark are indicated by the use of **or**. (Different terms in the mark scheme are shown by a / ; e.g. allow smooth / free movement.)

3. Marking points

3.1 Marking of Quality of Written Communication

Where *Quality of written communication* appears in the mark scheme, one mark is to be awarded for either of the following points:

- Using correct scientific terms
- Correct sequencing or linking of ideas or points

The mark scheme will specify which of the points is to be awarded in a particular question. A QoWC mark can be awarded for a scientific answer, even if it is not accurate. It cannot be awarded for a nonsensical or non-scientific answer.
On the script, the QoWC tick should be identified by a 'q' written next to it.

3.2 Marking of lists

This applies to questions requiring a set number of responses, but for which candidates have provided extra responses. The general principle to be followed in such a situation is that 'right + wrong = wrong'.

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols

Each error/contradiction negates each correct response. So, if the number of error/contradictions equals or exceeds the number of marks available for the question, no marks can be awarded.

However, responses considered to be neutral (indicated as * in example 1) are not penalised.

Example 1: What is the pH of an acidic solution? (1 mark)

Candidate	Response	Marks awarded
1	4,8	0
2	green, 5	0
3	red*, 5	1
4	red*, 8	0

Example 2: Name two planets in the solar system. (2 marks)

Candidate	Response	Marks awarded
1	Pluto, Mars, Moon	1
2	Pluto, Sun, Mars, Moon	0

3.3 Use of chemical symbols/formulae

If a candidate writes a chemical symbol/formula instead of a required chemical name, full credit can be given if the symbol/formula is correct and if, in the context of the question, such action is appropriate.

3.4 The marking of quantitative relationships

Full credit can be given for a correct quantitative relationship expressed in:

- named units;
- physical quantities;
- standard symbols;
- a combination of physical quantities and units.

No credit can be given for any quantitative relationship expressed in terms of:

- a combination of physical quantities, units and symbols;
- a diagram, e.g. the ohm's law triangle, unless the rest of the answer shows clearly that the candidate understands the relationships involved.

3.5 Marking procedure for calculations

3.5.1 Full marks can be given for a correct numerical answer, as shown in the column 'answers', without any working shown.
However:

- if the answer is incorrect, mark(s) can be gained by correct substitution/working and this is shown in the 'extra information' column;
- if the answer is correct, but an incorrect relationship is written in the working, then no marks can be awarded (see 3.5.2).

3.5.2 Where calculations are based on incorrectly recalled relationships, neither the incorrectly recalled relationship, nor the resulting calculation based on the incorrect relationship, will be credited.

3.6 Interpretation of 'it'

Answers using the word 'it' should be given credit only if it is clear that the 'it' refers to the correct subject.

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols

3.7 Errors carried forward

There should be no error carried forward from a previous answer which has been based on wrong science. Any error in the answers to a structured question should be penalised once only.

Examples

(a) A candidate who calculates average speed using speed = time/distance **and** then proceeds to use this incorrect answer to calculate an acceleration based on the correct quantitative relationship should be given credit for the use of the correct acceleration relationship but none for either numerical answer.

(b) A candidate who incorrectly calculates average speed using speed = distance/time and then proceeds to use this incorrect value to calculate an acceleration based on the correct quantitative relationship, should be given credit for the use of both correct quantitative relationships **and** for the correct substitution and use of the incorrect value in the calculation of the rate of acceleration.

Papers should be constructed in such a way that the number of times errors can be carried forward are kept to a minimum. Allowances for errors carried forward are most likely to be restricted to calculation questions and should be shown by the abbreviation e.c.f. in the marking scheme.

3.8 Phonetic spelling

The phonetic spelling of correct scientific terminology should be credited **unless** there is a possible confusion with another technical term.

3.9 Brackets

(…..) is used to indicate information which is not essential for the mark to be awarded but is included to help the examiner identify the sense of the answer required.

3.10 Interpretation of marginal points

There will be times when the answer is almost, but not quite, correct. Some examiners would award a mark while others would not. In any one script, an attempt should be made to balance these nearly correct answers by giving the mark on some occasions but not on others. If this is not done, the marking would end up being too lenient or too harsh.

3.11 Unexpected Correct Answers not in the Mark Scheme

The Examiner should use professional judgement to award credit where a candidate has given an unexpected correct answer which is not covered by the mark scheme. The Examiner should consult with the Team Leader to confirm the judgement. The Team Leader should pass this answer on to the Principal Examiner with a view to informing all examiners.

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols

Double Award
Foundation Tier 3462/3F

3462/3F Q1

question	answers	extra information	mark
(a)	comet	correct order only	1
	elliptical		1
	Milky Way		1
	Universe		1
(b)(i)	D A C B	allow **2** marks for two letters in the correct place allow **1** mark for one letter in the correct place	3
(ii)	A		1
total			8

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols


3462/3F Q2

question	answers	extra information	mark
(a)	95		1
(b)	alpha	accept correct symbol	1
(c)	any **two** from: • radiation is outside the body • radiation will not reach (living) cells • radiation absorbed by the air	 accept detector is on ceiling or high up the wall accept radiation cannot pass through the body / skin accept cannot pass through the plastic casing do **not** accept because it is alpha radiation – unless qualified do **not** accept does not give off harmful substance do **not** accept cannot pass through building materials etc.	2
(d)	less (than)		1
total			5

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols

3462/3F Q3

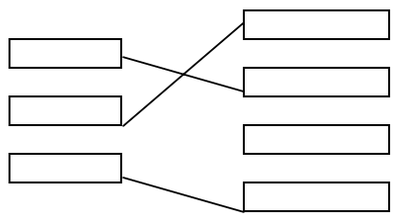question	answers	extra information	mark
(a)	generator	accept dynamo accept alternator	1
(b)(i)	1400	ignore units	1
(ii)	0.3 or 30%	any incorrect unit penalise **1** mark allow **1** mark for the correct use of 600 **or** 0.3% **or** 30	2
(c)	**1** mark for each correct link 	if more than 3 lines are drawn, mark only 3 lines starting with those that are incorrect	3
(d)(i)	110	no tolerance	1
(ii)	12	no tolerance	1
(iii)	wind speed may be too low to operate the generator	accept wind may not always blow accept power depends on wind speed accept does not generate if wind speed is too high accept does not generate if wind speed is above 12 (m/s) accept does not generate if wind speed is below 1.6 (m/s) accept it is unreliable do **not** accept answers referring to cost only	1
total			10

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols

3462/3F Q4

question	answers	extra information	mark
(a)	B E A D	allow **1** mark for each letter in the correct place, to a maximum of **3** marks	3
(b)	(a spark) may cause the (petrol vapour) to explode / ignite	accept petrol for (petrol vapour) accept catch fire for explode	1
	connect tanker to earth with a (conducting) wire / chain **or** earth the tanker	accept ground for earth	1
(c)	**Quality of written communication**	for a logical sequence	1
	any **two** from:		2
	• when current greater than fuse rating / value	accept when current too great for appliance do **not** accept 'if there is too much current' do **not** accept voltage or electricity	
	• fuse (becomes hot and) melts / burns out	accept fuse blows / breaks	
	• circuit is broken	accept circuit switched off this cannot score credit on its own	
total			8

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols

3462/3F Q5

question	answers	extra information	mark
(a)(i)	crust		1
(ii)	inner core is <u>solid</u> outer core is liquid	do **not** accept just rock inner core is denser / hotter than outer core gets **2** marks accept one is solid and one is liquid for **1** mark accept they are different densities for **1** mark wrong way round = **0** marks	1 1
(b)	seismograph		1
(c)	difficult to measure (slow) movement (1) of plates (1) dependent mark **or** difficult to measure friction / forces (1) between plates (1) dependent mark		1 1
(d)	geothermal		1
(e)(i)	5000		1
(ii)	2500		1
total			9

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols


3462/3F Q6

question	answers	extra information	mark
(a)	60		1
(b)	$5\frac{1}{2}$ hours	must include unit	1
(c)	30		1
(d)	30 minutes or $\frac{1}{2}$ hour	must include unit	1
(e)	D **and** E least steep part of the graph	accept finish for E accept correct numbers from axes with units accept covers smallest distance in a set time accept only moves 5 km in $1\frac{1}{2}$ hours (accept anything between 5 and 6) ignore horse is tired	1 1
total			6

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols



3462/3F Q7

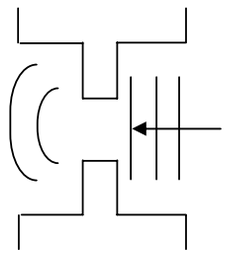question	answers	extra information	mark
(a)(i)	any **one** from: • (doctors) to see inside a patients body **or** endoscope • telephone cables • optical fibre / fibre optic lamps **or** (artificial) Christmas trees • data transfer **or** internet connection	 accept keyhole surgery do **not** accept flex **or** wires for cable accept decorative / ornamental lighting accept any feasible practical suggestion for taking light to a difficult to access place do **not** accept lighting unqualified do **not** accept lamp unqualified do **not** accept communications unless clarified	1
(ii)	(incident) ray angle greater than critical angle total internal reflection occurs	either order accept (incident) ray greater than 42° accept TIR do **not** accept just description of TIR	1 1
(b)(i)	waves shown diffracting in the correct direction 	ignore wavelength	1
(ii)	diffraction	accept diffract / diffracted	1
total			5

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols

3462/3F Q8

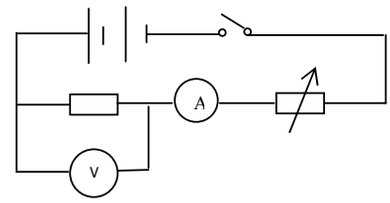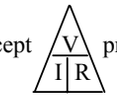question	answers	extra information	mark
(a)	all symbols correct	 accept push switch symbol switch may be open or closed any lines through symbols = **0** marks	1
	correct circuit drawn voltmeter must be across resistor only	polarity of cells not relevant provided they are joined correctly two cells are required in the diagram ignore the order of the components allow small gaps in circuit omission of any component = **0** marks	1
(b)(i)	potential difference = current × resistance	accept voltage or p.d. for potential difference accept $V = I \times R$ accept  provided subsequent use correct do **not** accept C for current	1
(ii)	2	 allow **1** mark for correct substitution wrong working loses both marks	2
(iii)	straight line drawn <u>through the origin</u> straight line passes through $I = 0.4, V =$ their (b)(ii) / 2 **and** 0.0	judge by eye this mark may be awarded if all points shown including these points are correct even if no line is drawn N.B. a curve scores **0** marks	1 1 dep
(c)	temperature <u>increases</u>	accept filament lamp / it gets <u>hotter</u> allow heat for temperature	1
total			8

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols

3462/3F Q9

question	answers	extra information	mark
(a)(i)	gamma rays	accept gamma accept correct symbol	1
(ii)	infra red	accept IR	1
(b)	ultraviolet <u>absorbed</u> by ink (energy) given out as light	 accept glows / luminous accept for **both** marks the ink is fluorescent do **not** accept answers in terms of uv being reflected	1 1
(c)	any **two** from: • UV can damage / kill / ionise / alter (normal) cells • change DNA structure **or** mutate • (normal) cells may become cancerous	 do **not** accept attacks cells **or** burns skin accept may cause (skin) cancer accept abnormal cell multiplication	2
(d)(i)	microwaves **and** infra red	both answers needed in either order do **not** accept heat for IR	1
(ii)	0.9	allow **1** mark for the <u>correct</u> use of 1.8 (kW) $(1.8 \times \frac{1}{2}$ or $1.8 \times 30)$ i.e. adding the correct 2 power values	2
total			9

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols


3462/3F Q10

question	answers	extra information	mark
(a)(i)	accelerating	accept getting faster accept speed / velocity increasing	1
(ii)	acceleration increases	accept velocity / speed increases more rapidly do **not** accept velocity / speed increases	1
(b)(i)	$\text{acceleration} = \frac{\text{change in velocity}}{\text{time (taken)}}$	accept $a = \frac{v - u}{t}$ **or** $a = \frac{v_1 - v_2}{t}$ do **not** accept velocity for change in velocity do **not** accept change in speed do **not** accept $a = \frac{v}{t}$	1
(ii)	15	allow **1** mark for an answer of 900 **or** for correct use of 540 seconds	2
(iii)	velocity includes direction	accept velocity is a vector (quantity) accept converse answer	1
(c)	force of gravity (between shuttle and Earth) plus correct orbital speed (makes shuttle move in a curve)	accept gravitational pull if used correctly accept forward motion **or** constant speed for orbital speed accept it is travelling fast enough accept for **2** marks the force of gravity provides the centripetal force	1 1
(d)	black is a good emitter of radiation **or** to limit the temperature rise inside the shuttle	accept heat for radiation accept the tiles are good insulation do **not** accept black absorbs heat on its own do **not** accept tiles are heat proof	1
total			9

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols

3462/3F Q11

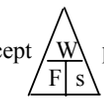question	answers	extra information	mark
(a)(i)	work (done) = force (applied) × distance (moved)	accept W = F × s or W = F × d accept  provided subsequent method is correct	1
(ii)	240 000 joules	allow **1** mark for correct substitution **or** correct use of 1200 (N) accept J do **not** accept j / Nm	2 1
(b)	800 (watts)	accept 0.8 kW accept their (a)(ii) ÷ 300 correctly evaluated for **2** marks allow **1** mark for correct substitution (a)(ii) ÷ 5 correctly evaluated for **1** mark	2
(c)(i)	any **one** from: • needs to raise the chair / lift • lifting more than one chair • energy transfer to the surroundings correctly qualified	 allow lifting more than 2 people implication of a heavier weight accept loss for transfer do **not** accept motor inefficient do **not** accept motor gets hot do **not** accept friction unless the location is specified as external to the motor	1
(ii)	electrical potential	accept electric **both** answers required for the mark	1
total			8

Copyright © 2004 AQA and its licensors

4.2.1.1 Standard circuit diagram symbols

3462/3F Q12

question	answers	extra information	mark
(a)	**Y** and **Z**		1
	they have the same number of protons **or** same atomic number	accept they have the same number of electrons **or** same number of protons **and** electrons allow only different in number of neutrons N.B. independent marks	1
(b)	**Quality of written communication**	for correct use of terms underlined in B **or** C Q ✓ Q X	1
	A – alpha particle passes straight through the empty space of the atom **or** it is a long way from the nucleus B – alpha particle deflected / repelled / repulsed by the (positive) nucleus C – alpha particle heading straight for the nucleus is deflected / repelled / repulsed backwards	describes 3 tracks correctly for **2** marks describes 2 or 1 track correctly for **1** mark do **not** accept hits the nucleus do **not** accept answers referring to refraction do **not** accept answers in terms of reflected backwards unless qualified in terms of repulsion mention of difference in charge on nucleus negates that track	max 2
total			5

Copyright © 2004 AQA and its licensors

Version 1.0: *27092005*

ASSESSMENT and QUALIFICATIONS ALLIANCE

General Certificate of Secondary Education

Physics 3451/F
Specification B

Mark Scheme

2005 examination – June series

Mark schemes are prepared by the Principal Examiner and considered, together with the relevant questions, by a panel of subject teachers. This mark scheme includes any amendments made at the standardisation meeting attended by all examiners and is the scheme which was used by them in this examination. The standardisation meeting ensures that the mark scheme covers the candidates' responses to questions and that every examiner understands and applies it in the same correct way. As preparation for the standardisation meeting each examiner analyses a number of candidates' scripts: alternative answers not already covered by the mark scheme are discussed at the meeting and legislated for. If, after this meeting, examiners encounter unusual answers which have not been discussed at the meeting they are required to refer these to the Principal Examiner.

It must be stressed that a mark scheme is a working document, in many cases further developed and expanded on the basis of candidates' reactions to a particular paper. Assumptions about future mark schemes on the basis of one year's document should be avoided; whilst the guiding principles of assessment remain constant, details will change, depending on the content of a particular examination paper.

Copyright © 2005 AQA and its licensors. All rights reserved.

Physics (Specification B)
Foundation Tier 3451/F

3451/F Q1

question	answers	extra information	mark
(a)(i)	less than	accept any correct indication	1
(ii)	more than	accept any correct indication	1
(b)	any **two** from: stays above the same place above the equator one orbit takes 24 hours	 do **not** accept stays in the same place do **not** accept goes around equator unless qualified do **not** accept orbit at same speed as Earth do **not** accept orbit at a constant speed accept has same angular speed / velocity as Earth	2
total			4

3451/F Q2

question	answers	extra information	mark
(a)	comet		1
(b)	large group / number / collection of stars	ignore reference to planets accept millions of stars do **not** accept thousands of stars do **not** accept loads of stars	1
(c)	giant supernova neutron		1 1 1
total			5

4.2.1.1 Standard circuit diagram symbols

3451/F Q3

question	answers	extra information	mark
(a)(i)	radio		1
(ii)	gamma	accept microwave accept infrared	1
(iii)	ultra violet		1
(iv)	microwaves		1
(b)	the same as		1
(c)	X-rays do not go through lead	references to gamma rays are incorrect accept lead protects them from the X-rays accept not exposed to X-rays	1
	lead stops / reduces risk of X-rays harming / damaging / killing (persons) <u>cells</u>	accept X-rays (may) cause cancer accept organs for cell do **not** accept references to electric shock do **not** accept stops bones of people showing on X-ray answers involving the horse wearing an apron are incorrect	1
	Quality of written communication	award for a sensible sequence of **two** points	1
total			8

4.2.1.1 Standard circuit diagram symbols

3451/F Q4

question	answers	extra information	mark
(a)	light electrical		1 1
(b)	15% **or** 0.15	correct substitution gains **1** mark only an answer of 15 with no unit **or** an incorrect unit gains **1** mark an answer of 0.15 given with a unit gains **1** mark	2
(c)	the ticket machine is a long way from other electricity supplies		1
(d)	any figure between 5 and 10 inclusive	unit not required but if given must match numerical answer	1
total			6

3451/F Q5

question	answers	extra information	mark
(a)(i)	radon (gas)	do **not** accept gas	1
(ii)	background		1
(b)	bigger	accept any word which means bigger	1
(c)	**Z** alpha will not pass through aluminium or lead	if Z is not given, the reason does not score accept alpha cannot go through metals / dense material accept there is nothing to stop the radiation accept alpha will not pass through aluminium do **not** accept alpha will not pass through lead do **not** accept alpha stopped by air	1 1
total			5

4.2.1.1 Standard circuit diagram symbols

3451/F Q6

question	answers	extra information	mark
(a)	loses negative charge / electrons	do **not** accept positive charge transfers to the comb do **not** accept friction	1
(b)	**A** attract		1
	B repel		1
	C attract		1
(c)	**F A D E**	allow **2** marks for 2 letters in the correct place allow **1** mark for 1 letter in the correct place	3
total			7

4.2.1.1 Standard circuit diagram symbols

3451/F Q7

question	answers	extra information	mark
(a)	all points correctly plotted	tolerance ± $\frac{1}{2}$ square on y axis only allow **1** mark for 3 correctly plotted points	2
	attempt made to draw a smooth curve	do **not** accept dot-to-dot line	1
(b)(i)	3 days ± 0.2 **or** any value correctly obtained using their graph line	if no line drawn in (a), answer must be exactly 3	1
(ii)	3 days or their (b)(i)		1
(c)	radon-222	accept radon **or** 222 accept alpha or 3.8 correct isotope required for reason to score	1
	has the shortest half-life	accept the others have longer half-lives	1
total			7

4.2.1.1 Standard circuit diagram symbols

3451/F Q8

question	answers	extra information	mark
(a)	fossils of Cynognathus are found in Africa and South America		1
	the shapes ……. almost fit together	only two boxes should be ticked deduct **1** mark for each additional box to a minimum mark of **0**	1
(b)	continental		1
	crust		1
	tectonic		1
total			5

4.2.1.1 Standard circuit diagram symbols




3451/F Q9

question	answers	extra information	mark
(a)	capacitor	accept condenser	1
	LDR	**or** light dependent resistor accept 'ldr', 'Ldr' etc.	1
	relay (normally open)	do **not** accept 'relay normally closed'	1
(b)(i)	battery	accept '(battery of) cells' do **not** accept 'battery / cell'	1
(ii)	LED	**or** light emitting diode accept 'led' or 'Led' do **not** accept just 'diode'	1
(iii)	B will light (but C will not)	accept '(only) B will work' accept 'one is on the other is off' do **not** accept 'C is on and B is off'	1
(iv)	any **one** from: B is connected the right way round (and C is not) a (light emitting) diode only allows (a significant) current to flow in one direction B's anode is connected to the positive side of the supply B's cathode is connected to the negative terminal	N.B. the candidate's answer to part (b)(iii) may include this mark but do **not** credit if the response to part (b)(iii) is incorrect or there is any other contradiction if (iv) is completely consistent with (iii) which is wrong, allow **1** mark	1
(c)(i)	first input / second input / output 0 / 0 / **0** 1 / 0 / **0** 0 / 1 / **0** 1 / 1 / **1**	**all** correct allow: OFF NO OFF NO OFF NO ON YES	1
(ii)	truth (table)		1

cont…

4.2.1.1 Standard circuit diagram symbols

3451/F Q9 cont…

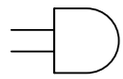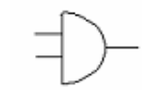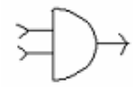(iii)		a Roman upper case D in any orientation without contacts is acceptable but if contacts are shown do **not** give the mark if there is any ambiguity or contradiction allow  	1
(d)	light sensor	**or** light dependent resistor **or** LDR accept 'ldr', Ldr' etc allow solar cell, photo cell	1
	NOT gate	accept 'Not gate' **or** 'not gate' if both correct but in the wrong order credit with **1** mark	1
total			12



4.2.1.1 Standard circuit diagram symbols

3451/F Q10

question	answers	extra information	mark
(a)(i)	rays continued to meet on the right hand side of the lens and beyond	must be straight lines from the right hand side of the lens ignore details through the lens allow if no arrows	1
	meet exactly on the axis	negate mark if contradictory arrow(s) added do not need to go beyond the focus for this mark	1
(ii)	(principal) focus	**or** focal (point)	1
(iii)	converging	**or** convex	1
(b)(i)	**A**		1
(ii)	rays seem to come from this point	**or** words to this effect **or** shows this on the diagram	1
(iii)	diverging	**or** concave	1
(c)	film	accept any unambiguous method of showing the correct response	1
	smaller than		1
	further away from		1
(d)	any **three** from: • real image can be put on a screen • virtual image cannot be put on a screen / film • virtual image is imaginary • real image is formed where (real) rays cross / converge • virtual image is where virtual / imaginary rays (seem to) come from • virtual image formed where virtual rays intersect / cross	allow film allow real image has light travelling through it **or** virtual image is where rays seem to come from	3
total			13

4.2.1.1 Standard circuit diagram symbols

3451/F Q11

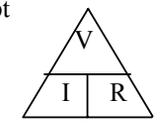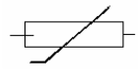question	answers	extra information	mark
(a)(i)	$A_1 = 0.5$ $A_4 = 0.5$	ignore any units allow **1** mark for $A_1 = A_4 \neq 0.5$	1 1
(ii)	the resistance of **P** is more than 20 Ω a smaller current goes through P / A_2 (than 20 Ω)	 dependent on getting 1st mark correct accept converse	1 1
(b)(i)	potential difference = current × resistance	accept pd / voltage for potential difference accept V = I × R, correct symbols and correct case only accept volts = amps × ohms accept  provided subsequent method is correct allow combination of physical quantities and named units allow voltage = I × R	1
(ii)	6	allow **1** mark for correct substitution	2
(iii)	6	accept their (b)(ii)	1
(c)	thermistor or  resistance goes down (as temperature of thermistor goes up)	accept correct circuit symbol allow phonetic spelling do **not** accept changes for goes down do **not** accept an answer in terms of current only answers in terms of other components are incorrect	1 1
total			10

4.2.1.1 Standard circuit diagram symbols

3451/F Q12

question	answers	extra information	mark
(a)(i)	larger the distance, greater the time	accept 'they are proportional' accept converse	1
(ii)	any value between 6 and 9 years inclusive		1
(b)(i)	carbon dioxide		1
(ii)	(Venus) has high**er** temperature (than Mercury)	accept has the high**est** temperature accept Venus is hotter / hottest do **not** accept has a high / very high temperature	1
	(Venus) further from the Sun than Mercury	accept 'Venus is not the closest planet to the Sun' answer in terms of greenhouse effect only, scores **0** marks	1
total			5

4.2.1.1 Standard circuit diagram symbols

3451/F Q13

question	answers	extra information	mark
(a)(i)	20		1
(ii)	convection		1
(iii)	fit draughtproof strips	accept lay carpet accept fit curtains accept close doors / windows / curtains accept any reasonable suggestion for reducing a draught 'double glazing' alone is insufficient	1
(b)	air is (a good) insulator **or** air is a poor conductor	accept air cavity / 'it' for air	1
	reducing heat transfer by <u>conduction</u>	accept stops for reduces ignore convection do **not** accept radiation do **not** accept answers in terms of heat being trapped	1
(c)(i)	most cost effective	accept it is cheaper or low<u>est</u> cost accept shortest payback time accept in terms of reducing heat loss by the largest amount do **not** accept it is easier ignore most heat is lost through the roof	1
(ii)	4		1
total			7

4.2.1.1 Standard circuit diagram symbols

3451/F Q14

question	answers	extra information	mark
(a)(i)	constant speed	do **not** accept normal speed do **not** accept it is stopped / stationary	1
	in a straight line	accept any appropriate reference to a direction constant velocity gains **2** marks 'not accelerating' gains **2** marks terminal velocity alone gets **1** mark	1
(ii)	goes down owtte	accept motorbike (it) slows down	1
(b)(i)	20 (m/s)	ignore incorrect units	1
(ii)	acceleration = change in velocity / time (taken)	do **not** accept velocity for change in velocity accept change in speed accept $a = \frac{v-u}{t}$ **or** $a = \frac{v_1 - v_2}{t}$ **or** $a = \frac{\Delta v}{t}$ do **not** accept $a = \frac{v}{t}$	1
(iii)	4 **or** their (b)(i) ÷ 5	allow **1** mark for correct substitution	2
	m/s^2	m/s/s **or** ms^{-2} **or** metres per second squared **or** metres per second per second	1
(c)	vehicle may skid / slide	loss of control / brakes lock / wheels lock accept greater stopping distance **or** difficult to stop	1
	due to reduced friction (between tyre(s) and road)	accept due to less grip do **not** accept no friction	1

cont…

4.2.1.1 Standard circuit diagram symbols

3451/F Q14 cont…

(d)	any **three** from: • increased speed • reduced braking force • slower (driver) reactions • poor vehicle maintenance • increased mass / weight of vehicle • poor road surface • more streamlined	do **not** accept night time / poor vision N.B. specific answers may **each** gain credit eg tiredness (1), drinking alcohol (1), using drugs (1), driver distracted (1) etc specific examples may **each** gain credit eg worn brakes or worn tyres etc accept large mass / weight of vehicle if candidates give three answers that affect stopping distance but not specific to increase award **1** mark only	3
total			13

4.2.1.1 Standard circuit diagram symbols

3451/F Q15

question	answers	extra information	mark
(a)(i)	arrow from centre of the ball **and** at right angles to the string **and** in the correct direction	arrow should point to the student's belt accept free-hand 'straight' line do **not** accept curved line	1
(ii)	increase increase increase	accept 'be stronger / bigger' accept 'be stronger / bigger' accept 'be stronger / bigger'	1 1 1
(b)	speed velocity direction	all **three** correct any two correct for **1** mark otherwise **0** marks	2
(c)(i)	centripetal	accept 'centripedal' and other minor misspellings do **not** accept anything which could be 'centrifugal'	1
(ii)	gravity	accept 'weight' accept 'force of attraction due to mass(es) (of the Moon and the Earth)'	1
(iii)	electron(s)		1
(iv)	electrostatic	accept 'electrical' do **not** accept just 'centripetal'	1
total			10


4.2.1.1 Standard circuit diagram symbols

3451/F Q16

question	answers	extra information	mark
(a)(i)	**X** at the centre of the lifebelt	measuring from the centre of **X**, allow 2 mm tolerance in any direction	1
(ii)	any **two** from: below the point of suspension at the centre (of the lifebelt) (because) the lifebelt / it is symmetrical	if X is on vertical line below the hanger (but not at centre) can gain the first point only accept '(vertically) below **Y**' accept 'in the middle' **or** (because) the mass / weight is evenly distributed	2
(b)	Nm **or** newton metre(s) 750	accept Newton metre(s) do **not** accept any ambiguity in the symbol ie NM, nM or nm (moment) = force × (perpendicular) distance (between line of action and pivot) **or** (moment) = 500 × 1.5 gains **1** mark	1 2
(c)	**Quality of written communication**: any **three** connected points from: low(er) <u>centre of mass / gravity</u> (more) <u>stable</u> less likely to fall over the <u>turning effect / moment</u> (of the weight of case) is less so the pull on her arm is less	for **2** of the underlined terms used in the correct context **or** <u>centre of mass / gravity</u> will be close(r) to the wheels / axle / ground **or** less <u>unstable</u> accept 'less likely to overturn' do **not** accept 'will not fall over' **or** so less effort is needed to hold the case ignore references to pulling the case	1 3
total			10

4.2.1.1 Standard circuit diagram symbols

3451/F Q17

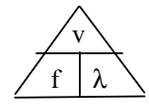question	answers	extra information	mark
(a)	any **two** from: • **amplitude** decreasing • **wavelength** increasing • **frequency** decreasing **Quality of written communication**	accept siren / sound getting quieter do **not** accept sound decreases accept pitch decreasing ignore reference to transverse wave ignore reference to speed contradictory statements within each point lose the mark all emboldened terms in candidate's answer used correctly	2 1
(b)(i)	ultrasound **or** ultrasonic		1
(ii)	wave speed = frequency × wavelength	accept speed / velocity for wave speed accept $v = f \times \lambda$ do **not** accept w for λ do **not** accept s for v accept  provided subsequent calculation shows a correct method	1
(iii)	339.2 **or** 340 **or** 339	allow **1** mark for using 212 000 allow **1** mark for correct substitution an answer of 0.3392 **or** 0.34 **or** 0.339 gains **1** mark only award full credit for a correct numerical answer with the unit changed to km/s	3
total			8

Version 1.0: 0906

ASSESSMENT and QUALIFICATIONS ALLIANCE

General Certificate of Secondary Education

Physics 3451/F
Specification B

Mark Scheme

2006 examination - June series

Mark schemes are prepared by the Principal Examiner and considered, together with the relevant questions, by a panel of subject teachers. This mark scheme includes any amendments made at the standardisation meeting attended by all examiners and is the scheme which was used by them in this examination. The standardisation meeting ensures that the mark scheme covers the candidates' responses to questions and that every examiner understands and applies it in the same correct way. As preparation for the standardisation meeting each examiner analyses a number of candidates' scripts: alternative answers not already covered by the mark scheme are discussed at the meeting and legislated for. If, after this meeting, examiners encounter unusual answers which have not been discussed at the meeting they are required to refer these to the Principal Examiner.


It must be stressed that a mark scheme is a working document, in many cases further developed and expanded on the basis of candidates' reactions to a particular paper. Assumptions about future mark schemes on the basis of one year's document should be avoided; whilst the guiding principles of assessment remain constant, details will change, depending on the content of a particular examination paper.

Copyright © 2006 AQA and its licensors. All rights reserved.

4.2.1.1 Standard circuit diagram symbols

Physics (Specification B)
Foundation Tier 3451/F

3451/F Q1

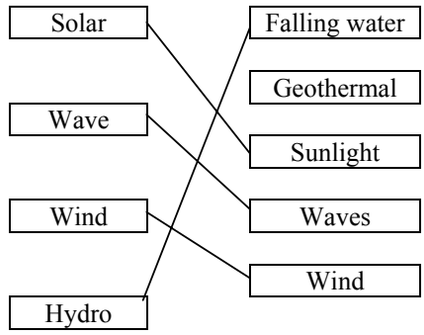question	answers	extra information	mark
(a)	4 correct lines drawn  	**1** mark for each correct line if more than 4 lines are drawn mark incorrect ones first. Mark only 4 lines	4
(b)	4		1
(c)(i)	nuclear		1
(ii)	(natural) gas	do **not** accept natural	1
total			7

4.2.1.1 Standard circuit diagram symbols

3451/F Q2

question	answers	extra information	mark
(a)(i)	ultra violet		1
(ii)	kill the cells	accept destroys the cells accept makes cells cancerous accept damage cells accept harms cells accept changes DNA accept cause cells to mutate accept skin cells for cells accept cause cancer do **not** accept skin for cells do **not** accept burns the cells	1
(b)(i)	the sunbed uses an alternating current (a.c.) supply		1
(ii)	10.8	accept **1** mark for correct substitution of power in W or kW and time in hours or seconds	2
total			5

4.2.1.1 Standard circuit diagram symbols

3451/F Q3

question	answers	extra information	mark
(a)(i)	M		1
(ii)	K		1
(iii)	J		1
(iv)	O		1
(b)(i)	billions of years		1
(ii)	red giant	any answer in terms of explosion or supernova is **incorrect**	1
	contracts / shrinks to	incorrect reference to black hole negates **1** mark	1
	white dwarf		1
total			8

4.2.1.1 Standard circuit diagram symbols

3451/F Q4

question	answers	extra information	mark
(a)(i)	A and C	**both** answers must be correct in either order	1
(ii)	A and B	**both** answers must be correct in either order	1
(iii)	same number of protons plus neutrons **or** same number of nucleons	accept number of particles in nucleus the same do **not** accept they add up to 6 unless qualified	1
(b)(i)	any **two** from: • boron - 12 • carbon - 14 • oxygen - 15 • lead - 209	**both** required both name **and** number must be given	1
(ii)	any **two** from: • boron - 11 • carbon - 12 • oxygen - 16 • lead - 207	**both** required both name **and** number must be given	1
(c)	alpha		1
total			6

4.2.1.1 Standard circuit diagram symbols

3451/F Q5

question	answers	extra information	mark
(a)	(good) insulator	accept does not conduct (electricity) accept does not conduct heat or electricity do **not** accept does not conduct heat outside is tough is insufficient	1
(b)	fuse		1
(c)	connect the green and yellow / earth wire	accept wires must be connected to screws	1
	swap the brown and blue wires round		1
total			4

3451/F Q6

question	answers	extra information	mark
(a)	fossils	answers can be in either order	1
	water		1
(b)	increased		1
(c)	radio telescope		1
total			4

4.2.1.1 Standard circuit diagram symbols

3451/F Q7

question	answers	extra information	mark
(a)(i)	electrical		1
	kinetic	accept movement	1
(ii)	heat	answers can be in either order	1
	sound		1
(b)(i)	360	accept **1** mark for correct substitution	2
(ii)	watt		1
(c)	the stairlift is not moving the stairlift is moving at constant speed	**both** answers are required for the mark	1
total			8

3451/F Q8

question	answers	extra information	mark
(a)(i)	(up) further **or** (up) faster	any reference to downwards movement loses credit accept <u>with</u> more force accept motion would increase	1
(ii)	down	accept the opposite way accept drop	1
(b)(i)	direct current		1
(ii)	Z		1
total			4

4.2.1.1 Standard circuit diagram symbols

3451/F Q9

question	answers	extra information	mark
(a)	level of radiation (detected) will not change	ignore reference to particles	1
	if thickness of aluminium changes	accept for **both** marks a specific example eg if the aluminium gets thicker the level of radiation detected stays the same. accept for **1** mark gamma will pass through aluminium	1
	QoWC for 2 points in a sensible sequence		1
(b)	S W T V	all in correct order accept **2** marks for 2 correct accept **1** mark for 1 correct	3
total			6

4.2.1.1 Standard circuit diagram symbols

3451/F Q10

<table>
<tr><th>question</th><th>answers</th><th>extra information</th><th>mark</th></tr>
<tr><td>(a)</td><td>thermistor(s)
LDR(s)
switch(es)
LED(s)
buzzer(s)
motor(s)</td><td>1 mark each
or light dependent resistor(s)
or light emitting diode(s)</td><td>6</td></tr>
<tr><td>(b)(i)</td><td><table><tr><th>1st input</th><th>2nd input</th><th>Output</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table></td><td>all correct</td><td>1</td></tr>
<tr><td>(ii)</td><td><table><tr><th>Input</th><th>Output</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table></td><td>both correct</td><td>1</td></tr>
<tr><td>(iii)</td><td><table><tr><th>1st input</th><th>2nd input</th><th>Output</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table></td><td>all correct</td><td>1</td></tr>
<tr><td>(c)(i)</td><td></td><td>do not credit any attempt which could equally well be a poorly drawn attempt at the symbol for a cell</td><td>1</td></tr>
<tr><td>(ii)</td><td>charge

increases</td><td>accept ‘electrons’
accept ‘energy
or gets bigger/larger</td><td>1

1</td></tr>
<tr><td>total</td><td></td><td></td><td>12</td></tr>
</table>

4.2.1.1 Standard circuit diagram symbols

3451/F Q11

question	answers	extra information	mark
(a)(i)	A		1
(ii)	B		1
(iii)	mass is larger	credit if the response is clear by some other means e.g. it is ringed	1
	wire is shorter	credit if the response is clear by some other means e.g. it is ringed	1
(b)	moment		1
	distance		1
(c)(i)	1		1
(ii)	5		1
(iii)	any **two** from • remove slotted mass(es) • slide (slotted) masses / weights nearer pivot • slide forcemeter away from the pivot • slide rod to the left	 **or** ….. to the left **or** ….. to the right **or** …. so that the slotted masses side is shorter **or** …. so that the forcemeter side is longer	2
(d)	centre of the rectangle	accept *2*mm tolerance any direction	1
	centre of the circle	accept *2*mm tolerance any direction	1
	on centre line and 10mm above base	accept *2*mm tolerance any direction	1
total			13

4.2.1.1 Standard circuit diagram symbols

3451/F Q12

question	answers	extra information	mark
(a)	0.05 (A)	ignore incorrect units if given accept 'the same' / 'the same as K' / 'the same as the other ammeter' do **not** accept 'same as the other meter'	1
(b)(i)	any **two** from: • two cells are joined + to +	answers in terms of current gain no marks accept one cell in the wrong way accept two cells are joined back-to-back accept two cells are joined – to – accept battery for cell do **not** accept answers in terms of all the cells or in terms of energy only	2
	• some of the cells potential difference is across the diode / ammeters / wires **or** the pd of the cells is shared by all components	accept voltage for pd do **not** accept using up pd	
	• the other components have a resistance	accept a named component / components / wire has a resistance	
	• cells not fully charged **or** cells partially run down	do **not** accept voltage of cells is less than 1.5 unless explained do **not** accept cells are not as powerful unless explained	
	• cells have an internal resistance		
(ii)	the diode has a (very) high resistance (in the reverse direction)		1
	a diode only conducts / allows current to flow in one direction	accept little / no current flows do **not** accept blocks / cuts flow	1

Continued

4.2.1.1 Standard circuit diagram symbols

3451/F Q12

question	answers	extra information	mark
(c)	**QoWC** for the use of the word resistance	annotate Q✓ Q✗ accept resistant	1
	accept increase / change / decrease throughout question but a contradiction loses **one** mark with change as neutral		
	as the pd / current increases / changes	accept voltage for pd must be correctly linked to at least one of the following points accept	1
	the temperature of the filament increases / changes	lamp / bulb for filament accept filament becomes hotter	1
	increasing / changing the **resistance** of the lamp		1
		accept for **1** mark only the filament lamp does not obey Ohm's law	
total			9

4.2.1.1 Standard circuit diagram symbols

3451/F Q13

question	answers	extra information	mark
(a)	0.5		1
	hertz	accept Hz but **not** HZ / hz / hZ accept (waves) per second **or** / sec **or** / s **or** s^{-1} **or** sec^{-1}	1
(b)	any **one** from: • any named part of the electromagnetic spectrum • S – waves / secondary waves • wave on a rope	 do **not** accept seismic waves / earthquake do **not** accept slinky unless clearly described	1
(c)	transverse – disturbance / vibration is perpendicular to the direction of energy transfer / wave travel	accept a correctly labelled diagram	1
	longitudinal – disturbance / vibration is parallel to the direction of energy transfer / wave travel	accept a correctly labelled diagram part explanation of the difference between transverse **and** longitudinal gains **1** mark	1
(d)(i)	TIR shown	needs to stay inside water jet ignore number of reflections **or** arrow heads lines straight by eye	1
(ii)	bigger than	any indication of correct answer	1
total			7


4.2.1.1 Standard circuit diagram symbols

3451/F Q14

question	answers	extra information	mark
(a)	W		1
	has only two states **or** is either on or off	accept discrete values only do **not** credit answer purely in terms of shape	1
(b)	any **one** from:		1
	• higher quality	accept clearer do **not** accept easier to read ignore faster accept <u>less</u> distortion **or** <u>less</u> weakening of signal strength do **not** accept no distortion / weakening on its own	
	• increased carrying capacity	accept more information can be sent **or** more channels	
	• errors can be rectified		
total			3

4.2.1.1 Standard circuit diagram symbols

3451/F Q15

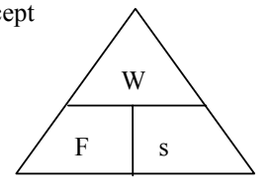question	answers	extra information	mark
(a)(i)	all points plotted accurately	accept **1** mark for 5 correct plots ± ½ small square on stopping distance	2
	line of best fit must be continuous	accept attempt at a reasonable curve does not need to go through 0 0 do **not** accept a straight line do **not** accept dot-to-dot	1
(ii)	4 to 6 (metres)	accept ecf from (a)(i) accept **1** mark for value taken correctly from graph at 25mph **or** correct method shown	2
(b)(i)	0.7 (s)	incorrect unit = 0 marks	1
(ii)	constant speed / velocity	accept (continued as) 30mph accept did not change / stayed the same accept no acceleration	1
(iii)	3.3(s)	penalise incorrect unit once only	1
(iv)	reaction time <u>increases</u> / is <u>longer</u> **or** thinking distance <u>increases</u>	do **not** accept reaction time slower **or** reactions are slower	1
	stopping distance / it <u>increases</u>	do **not** accept travels at constant speed for longer	1
(c)(i)	work done = force (applied) × distance (moved)	accept W = F × s or W = F × d accept  provided subsequent method is correct	1

Continued

4.2.1.1 Standard circuit diagram symbols

3451/F Q15

question	answers	extra information	mark
(ii) **E**	2100	accept 2.1 kilo accept **1** mark for using 7000 N	2
(iii)	2100 (joules)	accept their (c)(ii)	1
total			14

4.2.1.1 Standard circuit diagram symbols

3451/F Q16

question	answers	extra information	mark
(a)(i)	refraction		1
(ii)	it changes speed **or** change in density	accept it speeds up do **not** accept it slows down do **not** accept air is more dense than glass	1
(b)(i)	sound / waves <u>diffract</u> through the gap (in the wall) **or** over the wall **or** because the gate is open	do **not** accept reflection this only scores if first marking point is given accept for **1** mark only sound / waves go through the gap and <u>spread out</u> **or** diagram showing wave fronts spreading out from open gates if diagram is labelled as diffraction both marks can be scored	1 1
(ii)	less diffraction	accept no diffraction accept gates <u>absorb</u> sound / noise / waves accept gates <u>reflect</u> sound / noise / waves do **not** accept rebounds / stops / blocks out	1
total			5

4.2.1.1 Standard circuit diagram symbols

3451/F Q17

question	answers	extra information	mark
(a)	both rays brought to a focus at F on the right	do **not** have to be continued beyond F	1
	lines have been drawn **accurately** with a ruler	only credit if 1st mark credited do **not** credit if contradictory arrow(s) added	1
(b)	rays seem to come from a focus at G on the left and continued to the right of the lens	this mark is for the current idea of divergence	1
	lines have been drawn **accurately** with a ruler	only credit if 1st mark credited do **not** credit if contradictory arrow(s) added	1
(c)	…lens… …image… …object… …image… ...object… …lens…	lens as 1st and 6th words (1) image and object in the correct order 2nd and 3rd words (1) image and object in correct order 4th and 5th words (1)	max 3
(d)(i)	correct statement about real image real rays intersect / cross to form a real image **or** a real image can be formed on a screen **or** real image is (always) on the opposite side (of the lens) **or** real image is (always) upside down (to the object)	may be credited from a correct diagram	1
	correct statement about virtual / imaginary image virtual / imaginary rays intersect / cross to form a virtual image **or** a virtual / imaginary image cannot **or** virtual / imaginary image is (always) on the same side (of the lens) **or** virtual / imaginary image is (always) same way up (as the object)	may be credited from a correct diagram	1

Continued

4.2.1.1 Standard circuit diagram symbols

3451/F Q17

question	answers	extra information	mark
(ii)	**either** image needs to fall on / affect the film **or** image needs to fall on / affect the light sensors / charged coupled devices (CCDs) (in a digital camera / mobile phone) **or** image needs to cause a chemical reaction (in / on the film)		1
total			10

4.2.1.1 Standard circuit diagram symbols

3451/F Q18

<table>
<tr><th>question</th><th>answers</th><th>extra information</th><th>mark</th></tr>
<tr><td>(a)</td><td>AND (gate)

OR (gate)

NOT (gate)

LED or light emitting diode</td><td>accept ‘and’

accept ‘or’

accept ‘not’ or invert gate

accept ‘led’</td><td>1

1

1

1</td></tr>
<tr><td>(b)(i)</td><td>NOT (gate) and AND (gate)</td><td>both in either order or ‘(the) gates’

any additions lose the mark</td><td>1</td></tr>
<tr><td>(ii)</td><td><table><tr><th>Switch for fire</th><th>Tilt switch</th><th>Signal to relay</th></tr><tr><td>0</td><td>0</td><td>…0…</td></tr><tr><td>0</td><td>1</td><td>…0…</td></tr><tr><td>1</td><td>0</td><td>…1…</td></tr><tr><td>1</td><td>1</td><td>…0…</td></tr></table></td><td>all correct

allow off or no
off no
on yes
off no</td><td>1</td></tr>
<tr><td>(iii)</td><td>(relay) acts as / is a switch

either
small current from the electronic / control circuit / system (1)

large current through the output / (electric) fire (1)

or

full current through electronic control system (1)

may damage components / lead to overheating / electric shock (1)

QoWC for correct use of the scientific term ‘current’</td><td>accept implication that it works as a switch e.g. ‘turns on fire’

or ‘small current through the coil (of the relay)’

do not accept small current is turned into a large current

annotate Q✓ Q×

if answer in terms of voltage isolation / voltage/ p.d. accept QoWC mark for correct use</td><td>1

1

1

1</td></tr>
<tr><td>total</td><td></td><td></td><td>10</td></tr>
</table>

4.2.1.1 Standard circuit diagram symbols

AQA

GCSE
Additional Science / Physics
PH2FP
Mark scheme

4408/4403
June 2015

Version/Stage: 1.0: Final

4.2.1.1 Standard circuit diagram symbols

Mark schemes are prepared by the Lead Assessment Writer and considered, together with the relevant questions, by a panel of subject teachers. This mark scheme includes any amendments made at the standardisation events which all associates participate in and is the scheme which was used by them in this examination. The standardisation process ensures that the mark scheme covers the students' responses to questions and that every associate understands and applies it in the same correct way. As preparation for standardisation each associate analyses a number of students' scripts. Alternative answers not already covered by the mark scheme are discussed and legislated for. If, after the standardisation process, associates encounter unusual answers which have not been raised they are required to refer these to the Lead Assessment Writer.

It must be stressed that a mark scheme is a working document, in many cases further developed and expanded on the basis of students' reactions to a particular paper. Assumptions about future mark schemes on the basis of one year's document should be avoided; whilst the guiding principles of assessment remain constant, details will change, depending on the content of a particular examination paper.

Further copies of this mark scheme are available from aqa.org.uk

Copyright © 2015 AQA and its licensors. All rights reserved.
AQA retains the copyright on all its publications. However, registered schools/colleges for AQA are permitted to copy material from this booklet for their own internal use, with the following important exception: AQA cannot give permission to schools/colleges to photocopy any material that is acknowledged to a third party even for internal use within the centre.

4.2.1.1 Standard circuit diagram symbols

Mark Scheme

Information to Examiners

1. General

The mark scheme for each question shows:

- the marks available for each part of the question
- the total marks available for the question
- the typical answer or answers which are expected
- extra information to help the Examiner make his or her judgement and help to delineate what is acceptable or not worthy of credit or, in discursive answers, to give an overview of the area in which a mark or marks may be awarded
- the Assessment Objectives and specification content that each question is intended to cover.

The extra information is aligned to the appropriate answer in the left-hand part of the mark scheme and should only be applied to that item in the mark scheme.

At the beginning of a part of a question a reminder may be given, for example: where consequential marking needs to be considered in a calculation; or the answer may be on the diagram or at a different place on the script.

In general the right-hand side of the mark scheme is there to provide those extra details which confuse the main part of the mark scheme yet may be helpful in ensuring that marking is straightforward and consistent.

2. Emboldening

2.1 In a list of acceptable answers where more than one mark is available 'any **two** from' is used, with the number of marks emboldened. Each of the following bullet points is a potential mark.

2.2 A bold **and** is used to indicate that both parts of the answer are required to award the mark.

2.3 Alternative answers acceptable for a mark are indicated by the use of **or**. Different terms in the mark scheme are shown by a / ; eg allow smooth / free movement.

2.4 Any wording that is underlined is essential for the marking point to be awarded.

3. Marking points

3.1 Marking of lists

This applies to questions requiring a set number of responses, but for which students have provided extra responses. The general principle to be followed in such a situation is that 'right + wrong = wrong'.

Each error / contradiction negates each correct response. So, if the number of errors / contradictions equals or exceeds the number of marks available for the question, no marks can be awarded.

However, responses considered to be neutral (indicated as * in example 1) are not penalised.

4.2.1.1 Standard circuit diagram symbols

Example 1: What is the pH of an acidic solution? (1 mark)

Student	Response	Marks awarded
1	green, 5	0
2	red*, 5	1
3	red*, 8	0

Example 2: Name two planets in the solar system. (2 marks)

Student	Response	Marks awarded
1	Neptune, Mars, Moon	1
2	Neptune, Sun, Mars, Moon	0

3.2 Use of chemical symbols / formulae

If a student writes a chemical symbol / formula instead of a required chemical name, full credit can be given if the symbol / formula is correct and if, in the context of the question, such action is appropriate.

3.3 Marking procedure for calculations

Full marks can be given for a correct numerical answer, without any working shown.

However, if the answer is incorrect, mark(s) can be gained by correct substitution / working and this is shown in the 'extra information' column or by each stage of a longer calculation.

3.4 Interpretation of 'it'

Answers using the word 'it' should be given credit only if it is clear that the 'it' refers to the correct subject.

3.5 Errors carried forward

Any error in the answers to a structured question should be penalised once only.

Papers should be constructed in such a way that the number of times errors can be carried forward is kept to a minimum. Allowances for errors carried forward are most likely to be restricted to calculation questions and should be shown by the abbreviation e.c.f. in the marking scheme.

3.6 Phonetic spelling

The phonetic spelling of correct scientific terminology should be credited **unless** there is a possible confusion with another technical term.

3.7 Brackets

(.....) are used to indicate information which is not essential for the mark to be awarded but is included to help the examiner identify the sense of the answer required.

3.8 Accept / allow

Accept is used to indicate an equivalent answer to that given on the left-hand side of the mark scheme. Allow is used to denote lower-level responses that just gain credit.

3.9 Ignore / Insufficient / Do not allow

Ignore of insufficient is used when the information given is irrelevant to the question or not enough to gain the marking point. Any further correct amplification could gain the marking point.

Do **not** allow means that this is a wrong answer which, even if the correct answer is given, will still mean that the mark is not awarded.

4. Quality of Communication and levels marking

In Question **8c** students are required to produce extended written material in English, and will be assessed on the quality of their communication as well as the standard of the scientific response.

Students will be required to:
- use good English
- organise information clearly
- use specialist vocabulary where appropriate.

The following general criteria should be used to assign marks to a level:

Level 1: basic
- Knowledge of basic information
- Simple understanding
- The answer is poorly organised, with almost no specialist terms and their use demonstrating a general lack of understanding of their meaning, little or no detail
- The spelling, punctuation and grammar are very weak.

Level 2: clear
- Knowledge of accurate information
- Clear understanding
- The answer has some structure and organisation, use of specialist terms has been attempted but not always accurately, some detail is given
- There is reasonable accuracy in spelling, punctuation and grammar, although there may still be some errors.

Level 3: detailed
- Knowledge of accurate information appropriately contextualised
- Detailed understanding, supported by relevant evidence and examples
- Answer is coherent and in an organised, logical sequence, containing a wide range of appropriate or relevant specialist terms used accurately.
- The answer shows almost faultless spelling, punctuation and grammar.

4.2.1.1 Standard circuit diagram symbols

MARK SCHEME – GCSE ADDITIONAL SCIENCE / PHYSICS – PH2FP– JUNE 2015

Question	Answers	Extra information	Mark	AO / Spec. ref.	ID
1(a)	increases	accept reaches highest value do **not** accept increases and decreases	1	AO2 2.3.2	E
1(b)(i)	increases		1	AO1 2.3.2m	A
1(b)(ii)	increases		1	AO1 2.3.2m	A
1(c)	18 watt	allow **1** mark for correct substitution i.e. 12 x 1.5 provided no subsequent step accept W answer may be indicated in the list	2 1	AO2 2.4.2c AO1 2.4.2c	E
Total			**6**		

4.2.1.1 Standard circuit diagram symbols

Question	Answers	Extra information	Mark	AO / Spec. ref.	ID
2(a)	inside the Sun		1	AO1 2.6.2b	**A**
2(b)	fusion		1	AO1 2.6.2a	**G**
2(c)	energy		1	AO1 2.6.2f	**A**
Total			**3**		


4.2.1.1 Standard circuit diagram symbols

Question	Answers	Extra information	Mark	AO / Spec. ref.	ID
3(a)	3 (.0)	allow **1** mark for correct substitution i.e. 25 x 0.12 provided no subsequent step	2	AO2 2.1.5d	**E**
3(b)(i)	elastic potential kinetic	correct order only	1 1	AO1 2.1.5c 2.2	**G**
3(b)(ii)	increases to 80(mm) (or more)	accept any number greater than 75 an answer 'it (more than) doubles' gains both marks	1 1	AO3 2.1.5a	**E**
3(c)(i)	weight		1	AO1 2.1	**A**
3(c)(ii)	Downward speed increases		1	AO1 2.1.1e	**A**
Total			**8**		

4.2.1.1 Standard circuit diagram symbols

Question	Answers	Extra information	Mark	AO / Spec. ref.	ID
4(a)(i)	(3-pin) plug	do **not** accept plug socket	1	AO1 2.4.1d	**E**
4(a)(ii)	live and neutral		1	AO1 2.4.1e	**A**
4(a)(iii)	double		1	AO1 2.4.1j	**G**
4(b)	Direct current (d.c.) only		1	AO1 2.4.1a	**A**
4(c)(i)	live		1	AO1 2.4.1g	**G**
4(c)(ii)	too great a current flows	accept a surge of current accept too great a power accept an electrical fault do **not** accept voltage / energy / electricity too high	1	AO1 2.4.1g	**E**
4(c)(iii)	can be reset (disconnects circuit) faster	accept does not need replacing cheaper is insufficient does not melt is insufficient quicker to fix / replace is insufficient	1 1	AO2 2.4	**E**
Total			**8**		

4.2.1.1 Standard circuit diagram symbols

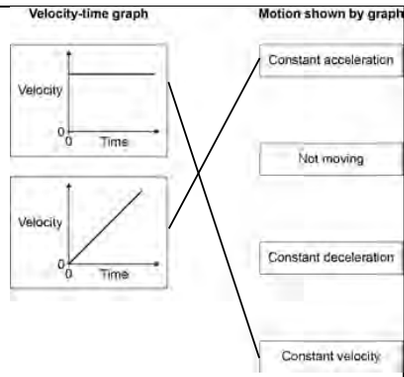Question	Answers	Extra information	Mark	AO / Spec. ref.	ID
5(a)		if more than one line is drawn from a graph then all those lines are wrong allow **1** mark for 1 correct line	2	AO1 2.1.2f	**G**
5(b)	speed		1	AO1 2.1.2d	**G**
5(c)(i)	2.25	allow **1** mark for correct substitution i.e. $a = \frac{9-0}{4}$ or $a = \frac{9}{4}$ provided no subsequent step	2	AO2 2.1.2e	**E**
5(c)(ii)	The air resistance increases		1	AO1 2.1.4a	**A**
5(d)	2000 J mass is half **or** kinetic energy depends on mass	 do **not** accept weight for mass	1 1	AO2 2.2.1g	**E**
Total			**8**		



4.2.1.1 Standard circuit diagram symbols

MARK SCHEME – GCSE ADDITIONAL SCIENCE / PHYSICS – PH2FP– JUNE 2015

Question	Answers	Extra information	Mark	AO / Spec. ref.	ID
6(a)	cell damage *or* cancer	accept kills/mutates cells radiation poisoning is insufficient ionising is insufficient	1	AO3 2.5.2g	**E**
6(b)(i)	any **one** from: • use tongs to pick up source • wear gloves • use (lead) shielding • minimise time (of exposure) • maximise distance (between source and teacher)	accept any other sensible and practical suggestion ignore reference to increasing / decreasing the number / thickness of lead sheets	1	AO3 2.5	**E**
6(b)(ii)	<u>background</u>		1	AO1 2.5.2b	**E**
6(c)(i)	curve drawn *from point 2,160*	do **not** accept straight lines drawn from dot to dot	1	AO2 2.5	**E**
6(c)(ii)	(also) increases	less radiation passes through is insufficient	1	AO3 2.5	**E**
6(c)(iii)	50	accept any value from 40 to 56 inclusive	1	AO3 2.5	**E**
6(d)	gamma only gamma (radiation) can pass through lead	 accept alpha **and** beta cannot pass through lead a general property of gamma radiation is insufficient	1 1	AO2 2.5.2e	**E**
Total			**8**		

4.2.1.1 Standard circuit diagram symbols

Question	Answers	Extra information	Mark	AO / Spec. ref.	ID
7(a)(i)	p.d. is (directly) proportional to current **or** gradient/slope is constant ***or*** the lines show constant resistance	accept lines are straight / diagonal	1	AO2 2.3.2d/e/g	**E**
7(a)(ii)	C for the same p.d. the current is the smallest	reason only scores if C is chosen accept lowest gradient **and** the gradient = 1/R	1 1	AO2 2.3.2i	**E**
7(b)(i) clip with table 1	ohm	accept correct symbol Ω accept an answer written in Table 1 if not given in answer space	1	AO1 2.3.2h	**E**
7(b)(ii)	K and L only length varies	reason only scores if both K and L are chosen accept type of metal and the diameter are the same	1 1	AO3 2.3.2	**E**
7(b)(iii)	measure the resistance of more wires made from different metals	accept test more (types of) metals measure the resistance of more wires is insufficient they only use two metals is insufficient	1	AO3 2.3.2	**E**

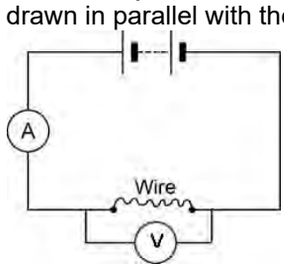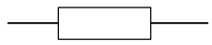7(c)(i)	voltmeter symbol correct and drawn in parallel with the wire 	accept voltmeter symbol correct and drawn in parallel with the battery	1	AO1 2.3.2c/f	**E**
7(c)(ii)	correct symbol drawn 	symbol must be rectangular	1	AO1 2.3.2c	**E**
Total			**9**		

Question	**Answers**	**Extra information**	**Mark**	**AO / Spec. ref.**	**ID**
8(a)	(an equal amount of) positive charge	do **not** accept charge on the atom / nucleus is positive	1	AO3 2.5.1	**E**
8(b)(i)	a (significant) number of alpha particles were scattered by more than 4° **or** alpha particles deflected backwards measurements / results could not be explained by 'plum pudding' model **or** measurements / results did not support predictions	accept (some) measurements / results were unexpected can be explained by the nuclear model is insufficient accept measurements / results did not support hypothesis	1 1	AO1 2.5 AO1	**E**
8(b)(ii)	many/(over)100 000 measurements / results taken	accept Rutherford(and Marsden) were respected scientists **or** scientists were respected accept measurements / results taken over several months the experiment was repeated many times is insufficient	1	AO3 2.5	**E**

4.2.1.1 Standard circuit diagram symbols

Question 8 continues on the next page . . .

Question	Answers	Extra information	Mark	AO / Spec. Ref.	ID
8(c)			6	AO1 2.5.1a/b/c	E

Marks awarded for this answer will be determined by the Quality of Written Communication (QWC) as well as the standard of the scientific response. Examiners should also refer to the information on page 5 and apply a 'best-fit' approach to the marking.

0 marks	Level 1 (1–2 marks)	Level 2 (3–4 marks)	Level 3 (5–6 marks)
no relevant content	A brief description is given with some particles correctly named	A description is given with all three particles named **plus either** the polarity of charge associated with the three particles **or** the relative mass of the three particles **or** the relative mass for one particle and the relative charge for one particle given	A more detailed description is given, naming the particles and polarity of charge **and either** the relative mass is given for at least two particles **or** the relative charge is given for at least two particles

examples of the points made in the response	extra information		
brief description contains protons, neutrons and electrons protons are positive electrons are negative neutrons are uncharged has a nucleus **relative charge** proton +1 electron – 1 neutron 0 **relative mass** proton 1 neutron 1 electron (about) 1/2000 **more detailed description** protons and neutrons make up the nucleus electrons orbit the nucleus electrons are in shells most of the atom is empty space nucleus occupies a very small fraction of the volume of the atom electrons orbit at a relatively large distance from the nucleus most of the mass of the atom is contained in the nucleus the nucleus as a whole is positively charged total number of protons in the nucleus equals the total number of electrons orbiting it in an atom	accept protons and neutrons have the same mass accept electrons have tiny / negligible mass zero mass is neutral		

Total		**10**

4.2.1.1 Standard circuit diagram symbols

Answer 21 · Examiner comments

June 2022 | 8463/1F | Original Q6

Question 6 (Low and standard demand)

06.1 35% of students recognised the resistors were connected in parallel with the power supply.

06.2 70% of students answered this question correctly.

06.3 70% of students answered this question correctly.

06.4 95% of students answered correctly, All students had the equations on the Physics Equations Sheet for the 2022 series.

06.5 70% of students answered correctly, scoring 3 marks. Students who did not gain any marks commonly multiplied the power and the energy values together. The first marking point was for the substitution, which students who couldn't rearrange often failed to score as they only wrote down 3600 × 1200 and their incorrect answer.

06.6 About 55% of students identified the correct circuit symbol.

4.2.1.1 Standard circuit diagram symbols

Answer 22 · Examiner comments June 2024 | 8463/1F | Original Q2

Question 2 (Low demand)

02.1 48% of students were able to recall the frequency of the UK mains electricity supply.

02.2 75% of students were able to recall the potential difference of the UK mains electricity supply.

02.3 94% of students scored 2 marks for this calculation question. For low demand calculations the equation is provided in the rearrangement needed to answer the question.

02.4 91% of students correctly identified the circuit symbol for a thermistor.

02.5 Only 24% of students chose the correct answer for this question, which tested how the potential difference is shared between components in a series circuit.

02.6 The question discriminated well between students. 12% of students scored 2 marks, while 33% scored 1 mark. The question tested whether students knew how the potential difference was shared between components with equal resistance. 'Because it's a series circuit' was insufficient to score the 2nd marking point.

02.7 80% of students scored 2 marks for this question, by calculating the change in resistance between two values of temperature.

Answer 23 · Examiner comments June 2024 | 8463/1F | Original Q7

Question 7 (Low / Standard demand)

07.1 42% of students answered this question correctly, identifying the colour of the insulation around the live wire.

07.2 Students were slightly more successful answering this question, with 48% correctly identifying the colour of the insulation around the neutral wire.

07.3 64% of students were able to identify the circuit symbol for a fuse.

07.4 92% of students scored 2 marks for this question. For low demand calculations the equation is provided in the rearrangement needed to answer the question.

07.5 72% of students multiplied numbers given in this standard demand calculation and scored 2 marks. Very few students attempted the unit conversion. Only 8% of students scored 3 marks for the correct final answer.

07.6 43% of students realised that the total energy would be greater.

4.2.1.1 Standard circuit diagram symbols

Answer 24 · Examiner comments June 2025 | 8463/1F | Original Q5

05.1

This question discriminated well with 44% of the students scoring 3 marks, 10 % of the students scoring 2 marks and 28 % of the students scoring 1 mark.

05.2

Nearly 70 % of the students scored the mark for identifying the circuit symbol for a fuse.

05.3

Most of the students scored 2 marks on this grade 1-3 calculation.

05.4

About 94 % of the students scored both marks on this calculation of resistance. Students who scored 0 marks usually rearranged the equation and multiplied the current^2 by the power. When students are provided with the equation at the point they need it in the exam, there is no need to rearrange the equation before using it as it is a grade 1-3 question.

05.5

Just over 60 % of the students scored 2 marks for correct comparisons between kettle A and kettle B. Many students did not read the instructions for the question and only ticked one box.